



Amateur Extra License Class

1



Amateur Extra Class

Chapter 5 Components and Building Blocks

2



Semiconductor Devices

Materials

- Atomic Structure.
 - Nucleus (Protons & Neutrons).
 - Electrons.
 - Orbits (Shells).
 - Valence electrons.
 - 8 Valence electrons completes a shell.
- Atomic number.
 - Number of protons in nucleus.
 - Number of electrons (non-ionized).

3



Semiconductor Devices

Periodic Table of the Elements

	1A																	0
1	H																	He
2	Li	Be											B	C	N	O	F	Ne
3	Na	Mg	III B	IV B	V B	VIB	VII B	VIII	IX	X	IB	IIB	Al	Si	P	S	Cl	Ar
4	K	Ca	Sc	Ti	V	Cr	Mn	Fe	Co	Ni	Cu	Zn	Ga	Ge	As	Se	Br	Kr
5	Rb	Sr	Y	Zr	Nb	Mo	Tc	Ru	Rh	Pd	Ag	Cd	In	Sn	Sb	Te	I	Xe
6	Cs	Ba	*La	Hf	Ta	W	Re	Os	Ir	Pt	Au	Hg	Tl	Pb	Bi	Po	At	Rn
7	Fr	Ra	+Ac	Rf	Ha	Sg	Ns	Hs	Mt	110	111	112	113					

* Lanthanide Series	Ce	Pr	Nd	Pm	Sm	Eu	Gd	Tb	Dy	Ho	Er	Tm	Yb	Lu
+ Actinide Series	Th	Pa	U	Np	Pu	Am	Cm	Bk	Cf	Es	Fm	Md	No	Lr

4



Semiconductor Devices

Materials

- Electrons in outer shell are called valence electrons.
 - Valence electrons allow atoms to interact with other atoms to form compounds.
 - Atoms want to have their outer shell of electrons filled.
 - Full shell = 8 electrons.
 - Atoms can share valence electrons with other atoms to fill their outer shell forming a compound.

5



Semiconductor Devices

Materials

- Atoms with fewer than 4 valence electrons are normally conductors (metals).
- Atoms with more than 4 valence electrons are normally non-conductors.
- Atoms with 4 valence electrons are normally semi-conductors.
 - Silicon
 - Germanium


6



Semiconductor Devices

Materials

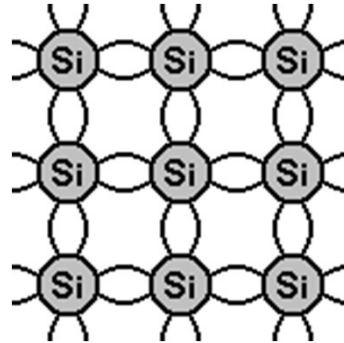- Atoms can arrange themselves into a regular pattern by sharing valence electrons to form a crystal.
- Crystals of pure silicon (Si) or germanium (Ge) are not normally good conductors.



7



Semiconductor Devices

Materials

- Crystals of pure semi-conductor atoms, such as silicon (Si), can have a precisely-controlled number of other atoms inserted into the crystal structure.
 - This process is called “doping”.
- Doping with atoms having 3 or 5 valence electrons causes the crystal to become more conductive.


8



Semiconductor Devices

Materials

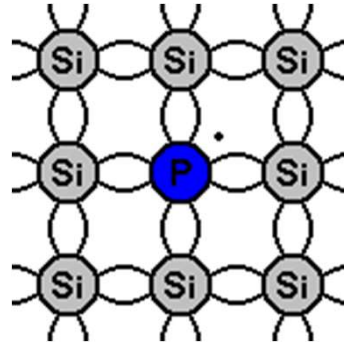- Adding an element with 5 valence electrons (donor impurity) creates N-type material.
 - Excess free electrons.
- Typical donor impurities:
 - Arsenic
 - Antimony
 - Phosphorus




9



Semiconductor Devices

Materials

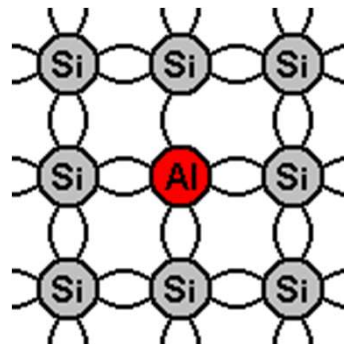- Adding an element with 3 valence electrons (acceptor impurity) creates P-type material.
 - Shortage of free electrons (holes).
- Typical acceptor impurities:
 - Aluminum
 - Gallium
 - Indium



10



Semiconductor Devices

Materials

- Majority Charge Carriers.
 - N-Type Material = Electron
 - P-Type Material = Hole
- Other semiconductor materials.
 - Gallium-Arsenide (GaAs).
 - LED's
 - Microwave frequencies.
 - Gallium-Arsenide-Phosphide (GaAsP).
 - LED's

11

E6A02 -- Which of the following semiconductor materials contains excess free electrons?

- A. N-type
- B. P-type
- C. Bipolar
- D. Insulated gate

12

E6A04 -- What is the name given to an impurity atom that adds holes to a semiconductor crystal structure?

- A. Insulator impurity
- B. N-type impurity
- C. Acceptor impurity
- D. Donor impurity

13



Semiconductor Devices

Junction Diodes

- A diode allows current to flow in one direction and resists current flow in the other direction.
- Two terminals:
 - Anode
 - Cathode.
- Electrons flow from cathode to anode.
- Holes flow from anode to cathode.


14



Semiconductor Devices

Junction Diodes

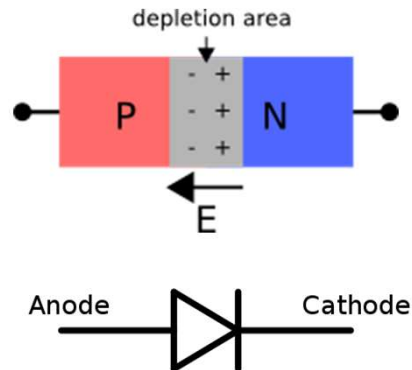- With no voltage applied, electrons & holes combine at the junction forming a depletion region.




15



Semiconductor Devices

Junction Diodes

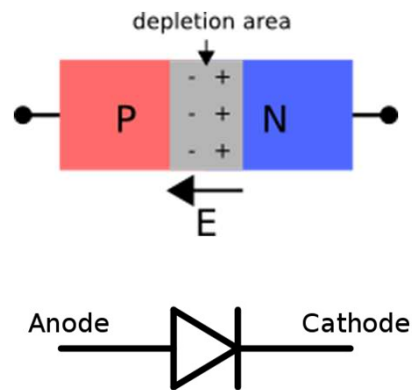- A positive voltage applied to anode will attract electrons in the N-type material.
 - The depletion area collapses.
 - Electrons flow from the N-type material to the P-type material.




16



Semiconductor Devices

Junction Diodes

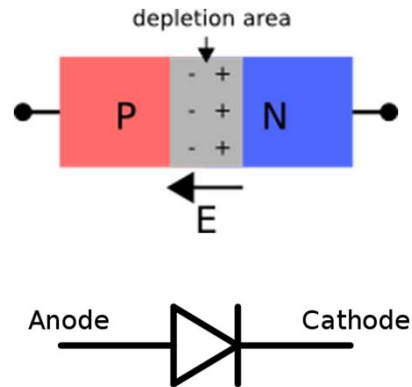- A negative voltage applied to anode will repel electrons in the N-type material.
 - The depletion area gets wider.
 - No electron flow.



17



Semiconductor Devices

Junction Diodes

- Forward Voltage Drop – Minimum forward voltage required for current to flow.
 - Silicon = 0.7 Volts (approx.)
 - Germanium = 0.3 Volts (approx.)
 - GaAs & GaAsP = 1.2 Volts to 1.5 Volts (approx.)

18



Semiconductor Devices

Junction Diodes

- Diode Ratings.
 - Peak Inverse Voltage (PIV).
 - Avalanche voltage.
 - Maximum Average Forward Current.
 - Maximum Allowable Junction Temperature.

Note: The most common result of a failed semiconductor junction is a short circuit.

19

E6A03 -- Why does a PN-junction diode not conduct current when reverse biased?

- A. Only P-type semiconductor material can conduct current
- B. Only N-type semiconductor material can conduct current
- ➔ C. Holes in P-type material and electrons in the N-type material are separated by the applied voltage, widening the depletion region
- D. Excess holes in P-type material combine with the electrons in N-type material, converting the entire diode into an insulator

20

E6A03 -- What is the failure mechanism when a junction diode fails due to excessive current?

- A. Excessive inverse voltage
- B. Excessive junction temperature
- C. Insufficient forward voltage
- D. Charge carrier depletion

21



Semiconductor Devices

Schottky Barrier Diodes

- P-type material replaced with a layer of metal.
 - Point-Contact Diodes.
 - Hot-Carrier Diodes.
- Lower forward voltage drop.
 - Less power dissipation.
 - Power supplies.




22



Semiconductor Devices

Schottky Barrier Diodes

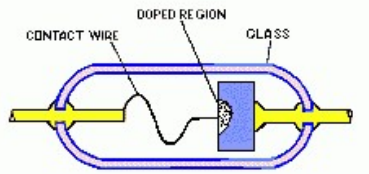- Point-Contact Diodes.
 - Very low junction capacitance.
 - Very low current.
 - Better for VHF & UHF detectors than normal junction diode.




23



Semiconductor Devices

Schottky Barrier Diodes

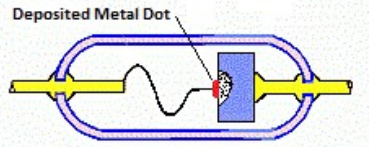- Hot-Carrier Diodes.
 - Similar to point-contact diode.
 - More stable mechanically.
 - Lower contact resistance → Higher current capability.
 - Better for VHF & UHF detectors than normal junction diode.



24

E6B02 -- What is an important characteristic of a Schottky diode as compared to an ordinary silicon diode when used as a power supply rectifier?

- A. Much higher reverse voltage breakdown
- B. Controlled reverse avalanche voltage
- C. Enhanced carrier retention time
- D. Less forward voltage drop

25

E6B08 -- Which of the following is a Schottky barrier diode?

- A. Metal-semiconductor junction
- B. Electrolytic rectifier
- C. PIN junction
- D. Thermionic emission diode

26

E6B09 -- What is a common use for point contact diodes?

- A. As a constant current source
- B. As a constant voltage source
- C. As an RF detector
- D. As a high voltage rectifier

27



Semiconductor Devices

Zener Diodes

- Operates with reverse bias.
- Operates at avalanche voltage.
- Large change in avalanche current results in small change in voltage.
- Designed to withstand avalanche current with proper heat sink.



28

E6B01 -- What is the most useful characteristic of a Zener diode?

- A. A constant current drop under conditions of varying voltage
- B. A constant voltage drop under conditions of varying current
- C. A negative resistance region
- D. An internal capacitance that varies with the applied voltage

29



Semiconductor Devices

Varactor Diodes

- Operates with reverse bias.
- Varying voltage varies junction capacitance.
 - Changes width of depletion region.
 - A few picofarads to >100 pF.
- Used for variable-frequency oscillators & for FM modulators.



30

E6B04 -- What type of semiconductor device is designed for use as a voltage-controlled capacitor?

- A. Varactor diode
- B. Tunnel diode
- C. Silicon-controlled rectifier
- D. Zener diode

31



Semiconductor Devices

PIN Diodes

- 3rd layer of undoped (intrinsic) material.
- Forward resistance varies with forward bias voltage.
 - More voltage → lower resistance.
- Used for RF attenuation & switching.



32

E6B05 -- What characteristic of a PIN diode makes it useful as an RF switch?

- A. Extremely high reverse breakdown voltage
- B. Ability to dissipate large amounts of power
- C. Reverse bias controls its forward voltage drop
- D. Low junction capacitance

33

E6B11 -- What is used to control the attenuation of RF signals by a PIN diode?

- A. Forward DC bias current
- B. A sub-harmonic pump signal
- C. Reverse voltage larger than the RF signal
- D. Capacitance of an RF coupling capacitor


34



Semiconductor Devices

Diodes, Transistors, and Integrated Circuits.

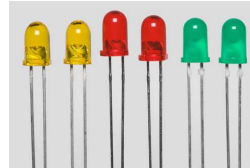- Light-Emitting Diodes (LEDs).
 - Special types of diodes that emit light from the junction when current flows (forward bias).
 - Color of the light determined by the type of semi-conductor material used.
 - Commonly used as visual indicators.



35

E6B03 -- What type of bias is required for an LED to emit light?


- A. Reverse bias
- B. Forward bias
- C. Zero bias
- D. Inductive bias

36

E6B10 -- In Figure E6-2, what is the schematic symbol for a light-emitting diode?

- A. 1
- B. 5
- C. 6
- D. 7

Figure E6-2

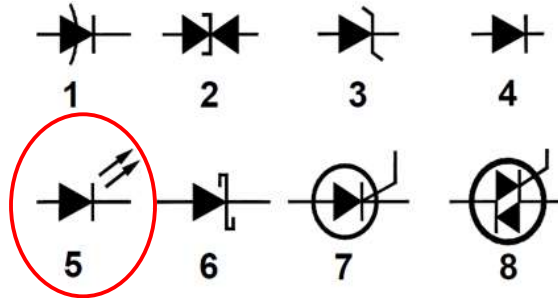


37



Semiconductor Devices

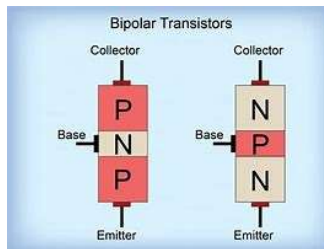- Bipolar Transistors
 - Adding another doped layer to a P-N junction diode results in a device capable of amplifying signals.




38



Semiconductor Devices

- Bipolar Transistors

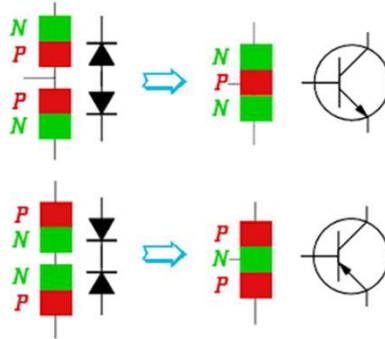



39



Semiconductor Devices

- Bipolar Transistors

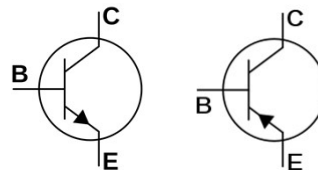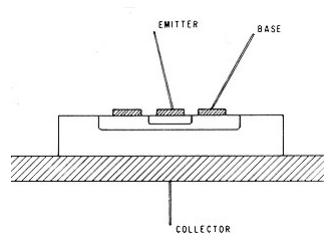- 3 doped layers.
 - N-P-N.
 - P-N-P.
- 3 terminals.
 - Collector.
 - Base.
 - Emitter.



40



Semiconductor Devices

- Bipolar Transistors
 - The base region is very thin.
 - The base-emitter junction is forward biased.
 - The collector-base junction is reverse biased.
 - A small current flowing through the base-emitter junction causes a large current to flow through the collector-base junction.
 - A bipolar transistor has low input impedance.
 - A bipolar transistor has low output impedance.

41



Semiconductor Devices

- Bipolar Transistors
 - Transistor characteristics.
 - Current gain (β).
 - $\beta = I_C / I_B$
 - Alpha (α).
 - $\alpha = I_C / I_E$

42



Semiconductor Devices

- Bipolar Transistors
 - Transistor characteristics.
 - Alpha Cut-off Frequency.
 - The frequency at which the common-base current gain drops to 0.707 times the value at 1 kHz.
 - Practical upper frequency limit for common-base amplifier.
 - Beta Cut-off Frequency.
 - The frequency at which the common-emitter current gain drops to 0.707 times the value at 1 kHz.
 - Practical upper frequency limit for common-emitter amplifier.

43



Semiconductor Devices

- Bipolar Transistors
 - Transistor characteristics.
 - Saturation – A bi-polar transistor is said to be “saturated” when an additional increase in base current does not result in an additional increase in collector current.
 - Cut-off – A bi-polar transistor is said to be “cut off” if there is insufficient base current to allow any collector current to flow.

44



Semiconductor Devices

- Bipolar Transistors
 - Transistor characteristics.
 - Since the base-emitter junction is a forward-biased diode, it will have a forward voltage drop when the transistor is biased “on” and there is collector-to-emitter current flow.
 - Germanium transistor: approximately 0.3v
 - Silicon transistor: approximately 0.6 to 0.7 volts


45

E6A06 -- What is the beta of a bipolar junction transistor?

- A. The frequency at which the current gain is reduced to 0.707
- B. The change in collector current with respect to base current
- C. The breakdown voltage of the base to collector junction
- D. The switching speed


46

E6A07 -- Which of the following indicates that a silicon NPN junction transistor is biased on?

- A. Base-to-emitter resistance of approximately 6 to 7 ohms
- B. Base-to-emitter resistance of approximately 0.6 to 0.7 ohms
- C. Base-to-emitter voltage of approximately 6 to 7 volts
-  D. Base-to-emitter voltage of approximately 0.6 to 0.7 volts

47

E6A08 -- What term indicates the frequency at which the grounded-base current gain of a transistor has decreased to 0.7 of the gain obtainable at 1 kHz?

- A. Corner frequency
- B. Alpha rejection frequency
- C. Beta cutoff frequency
-  D. Alpha cutoff frequency

48



Semiconductor Devices

Field Effect Transistors

- Field effect transistors or FETs differ from bipolar transistors.
 - An electric field (voltage) controls the current flow.
 - Two common types of FETs:
 - Junction field effect transistor (JFET).
 - Metal oxide semiconductor field effect transistor (MOSFET).
 - Both types of FETs have a very high input impedance.
 - JFET typically >10 megohm.
 - MOSFET typically >100 megohm.



49



Semiconductor Devices

Field Effect Transistors

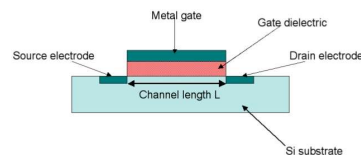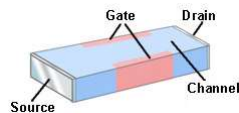- The gate voltage controls the channel current.
- Gain is measured in transconductance.
 - Unit of measurement is Siemens.
 - $G = I_D / V_G$



50



Semiconductor Devices

Field-Effect Transistors



- JFETs.
 - Junction Field-Effect Transistor.
 - A reverse-biased voltage between the gate & source junction controls the source-drain current.
 - Gate terminal is always reverse-biased.
 - Very little gate current flow.
 - High input impedance.
 - Low output impedance.

51



Semiconductor Devices

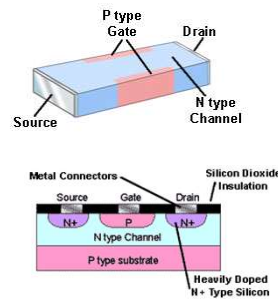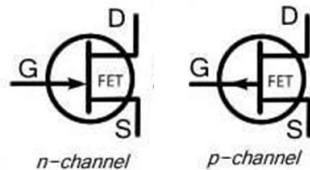- Field-Effect Transistors
 - JFETs.
 - Junction Field-Effect Transistor.



52



Semiconductor Devices

Field-Effect Transistors

- MOSFET.
 - Metal Oxide Semiconductor Field-Effect Transistor.
 - Gate is insulated from the source-drain channel by a layer of metal oxide.
 - No gate current flow.
 - Extremely high input impedance.
 - Susceptible to damage from static discharge.
 - Often have internal Zener diodes to protect gate.
 - Low output impedance.


53



Semiconductor Devices

Field-Effect Transistors

- MOSFETs.

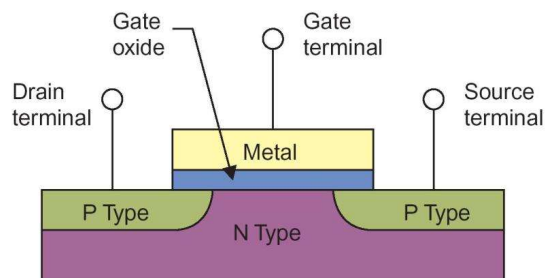

54



Semiconductor Devices

Field-Effect Transistors

- Enhancement and depletion mode FET's.
 - Enhancement mode.
 - $V_G = 0 V_{DC} \rightarrow$ No source-drain current flow.
 - Increasing gate voltage \rightarrow larger source-drain current.
 - JFETs are always enhancement mode.
 - Depletion mode.
 - $V_G = 0 V_{DC} \rightarrow$ Maximum source-drain current flow.
 - Increasing gate voltage \rightarrow smaller source-drain current.




55



Semiconductor Devices

Field-Effect Transistors

- MOSFETs.

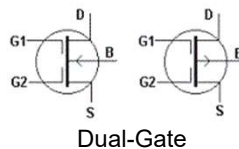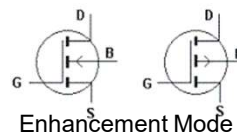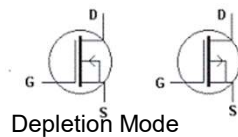

56

E6A05 -- How does DC input impedance at the gate of a field-effect transistor compare with the DC input impedance of a bipolar transistor?

- A. They are both low impedance
- B. An FET has lower input impedance
- C. An FET has higher input impedance
- D. They are both high impedance

57

E6A09 -- What is a depletion-mode FET?


- A. An FET that exhibits a current flow between source and drain when no gate voltage is applied
- B. An FET that has no current flow between source and drain when no gate voltage is applied
- C. Any FET without a channel
- D. Any FET for which holes are the majority carriers

58

E6A10 -- In Figure E6-1, what is the schematic symbol for an N-channel dual-gate MOSFET?

- A. 2
- B. 4
- C. 5
- D. 6

Figure E6-1

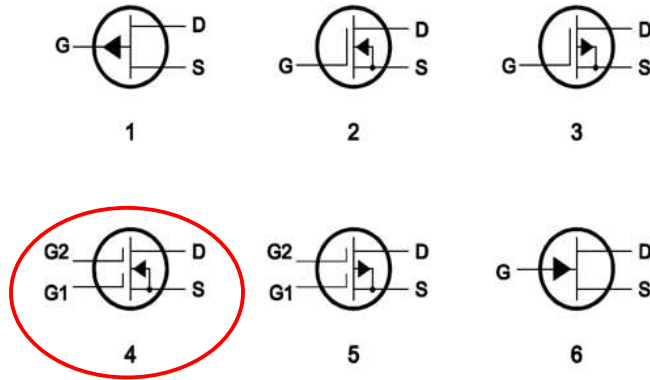


59

E6A11 -- In Figure E6-1, what is the schematic symbol for a P-channel junction FET?

- A. 1
- B. 2
- C. 3
- D. 6

Figure E6-1

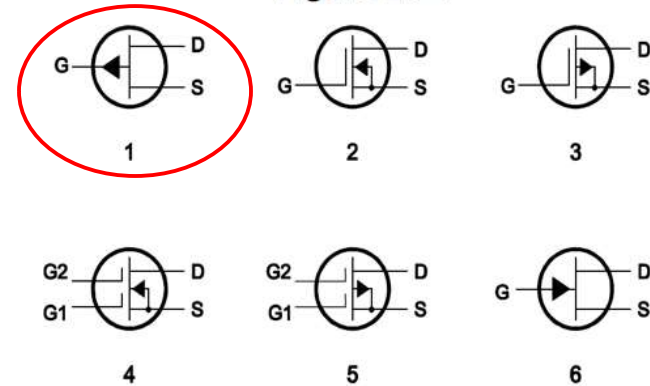

60

E6A12 -- Why do many MOSFET devices have internally connected Zener diodes on the gate?

- A. To provide a voltage reference for the correct amount of reverse-bias gate voltage
- B. To protect the substrate from excessive voltages
- C. To keep the gate voltage within specifications and prevent the device from overheating
- D. To reduce the chance of static damage to the gate

61



Semiconductor Devices

RF Integrated Devices

- Monolithic microwave integrated circuit (MMIC).
 - Silicon & germanium semiconductors do not perform well in the lower UHF range & higher frequencies.
 - Poor electron mobility.
 - MMICs are constructed of Gallium Arsenide (GaAs) or Gallium Nitride (GaN) which have higher electron mobility.
 - MMICs are commonly used as low-level amplifiers at VHF, UHF, & microwave frequencies.

62



Semiconductor Devices

RF Integrated Devices


- Monolithic microwave integrated circuit (MMIC).
 - MMICs are commonly used as low-level amplifiers at VHF, UHF, & microwave frequencies.
 - MMICs usually have input & output impedances of 50Ω .
 - MMICs have a low noise figure.
 - Typically 2.0 dB.

63



Semiconductor Devices

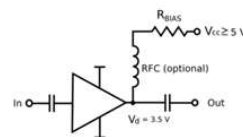- RF Integrated Devices
 - MMICs have 4 terminals.
 - Input connection.
 - Output connection.
 - 2 ground connections.
 - DC power is applied to the output terminal through a resistor and/or an RF choke.



- 1 - Input
- 2 - Ground (GND)
- 3 - Output
- 4 - Ground (GND)

64



Semiconductor Devices

RF Integrated Devices

- Microstrip construction.
 - Conventional construction techniques have too much stray inductance and are not suitable for use above the lower UHF frequencies.
 - Special construction techniques, called microstrip, are used to reduce this problem.

65



Semiconductor Devices

RF Integrated Devices

- Microstrip Construction.
 - Uses a double-sided PCB.
 - One side of the PCB is a ground plane.
 - Precisely-sized traces form 50 Ω transmission line segments.
 - Components are soldered directly to the transmission line segments.




66



Semiconductor Devices

RF Integrated Devices

- Microstrip Construction.

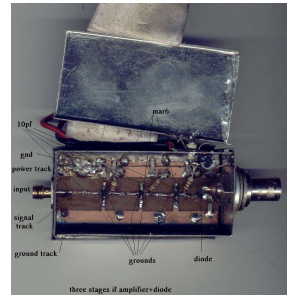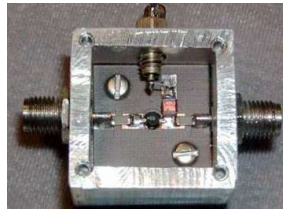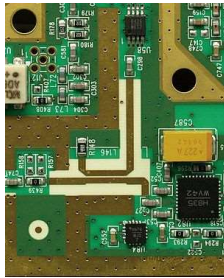


67

E5D03 -- What is microstrip?

- A. Lightweight transmission line made of common zip cord
- B. Miniature coax used for low power applications
- C. Short lengths of coax mounted on printed circuit boards to minimize time delay between microwave circuits
- ➔ D. Precision printed circuit conductors above a ground plane that provide constant impedance interconnects at microwave frequencies


68

E6A01 -- In what application is gallium arsenide used as a semiconductor material?

- A. In high-current rectifier circuits
- B. In high-power audio circuits
-  C. In microwave circuits
- D. In very low frequency RF circuits


69

E6E01 -- Why is gallium arsenide (GaAs) useful for semiconductor devices operating at UHF and higher frequencies?

- A. Higher noise figures
-  B. Higher electron mobility
- C. Lower junction voltage drop
- D. Lower transconductance


70

E6E03 -- Which of the following materials is likely to provide the highest frequency of operation when used in MMICs?

- A. Silicon
- B. Silicon nitride
- C. Silicon dioxide
-  D. Gallium nitride

71

E6E04 -- What is the most common input and output impedance of circuits that use MMICs?

-  A. 50 ohms
- B. 300 ohms
- C. 450 ohms
- D. 10 ohms

72

E6E05 -- Which of the following noise figure values is typical of a low-noise UHF preamplifier?

- A. 2 dB
- B. -10 dB
- C. 44 dBm
- D. -20 dBm


73

E6E06 -- What characteristics of the MMIC make it a popular choice for VHF through microwave circuits?

- A. The ability to retrieve information from a single signal even in the presence of other strong signals.
- B. Plate current that is controlled by a control grid
- C. Nearly infinite gain, very high input impedance, and very low output impedance
- D. Controlled gain, low noise figure, and constant input and output impedance over the specified frequency range


74

E6E07 -- What type of transmission line is used for connections to MMIC?

- A. Miniature coax
- B. Circular waveguide
- C. Parallel wire
-  D. Microstrip

75

E6E08 -- How is power supplied to the most common type of MMIC)?

-  A. Through a resistor and/or RF choke connected to the amplifier output lead
- B. MMICs require no operating bias
- C. Through a capacitor and RF choke connected to the amplifier input lead
- D. Directly to the bias-voltage (VCC IN) lead

76



Break



77



Optoelectronics

Photoconductivity

- Photoconductive effect.
 - Light striking a photosensitive material knocks electrons loose, thereby increasing the conductivity (lower resistance).
 - The photoconductive effect is most pronounced for crystalline semiconductors.
 - Cadmium-Sulfide: Visible light.
 - Lead-Sulfide: Infra-red light.
 - **ALL** semiconductor junctions exhibit the photoconductive effect.



78



Optoelectronics

Optoelectronic Components

- Most semiconductor devices are enclosed in a metal or plastic package to prevent the photoconductive effect from ambient light from affecting the operation of the device.
- Optoelectronic semiconductors have a transparent case or a window in the case to allow ambient light to reach the junction & alter the operation of the device.


79



Optoelectronics

Optoelectronic Components

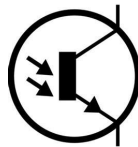- Phototransistor.
 - A transistor in a package that allows light to hit the junction.
 - The transistor turns on when it is exposed to light.
 - An external base connection may or may not be provided.



80





Optoelectronics

- Optoelectronic Components

- Optocouplers and optoisolators.

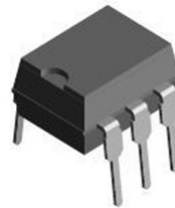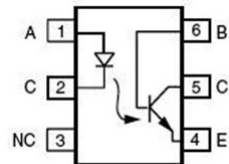- An LED & a phototransistor in the same package
 - Very high impedance between the light source & the phototransistor.
 - A high degree of isolation between the control circuit & the controlled circuit.
 - Functions as a solid-state relay.



81




Optoelectronics

- Optoelectronic Components

- Optocouplers and optoisolators.

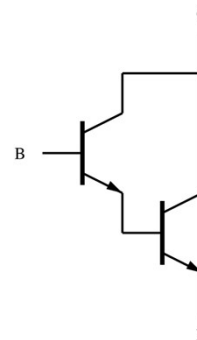- The main parameter of interest is the current transfer ratio (CTR).
 - The ratio of output current to input current.
 - Can use a Darlington phototransistor to increase the CTR.



82



Optoelectronics

- Optoelectronic Components
 - Optocouplers and optoisolators.
 - Sometimes a separate LED & phototransistor separated by a small gap are used.
 - This allows the detection of the presence or the absence of an object.
 - Can work by an object interrupting the light from the LED or by the object reflecting the light from the LED.




83



Optoelectronics

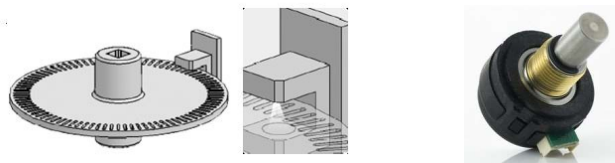- Optoelectronic Components
 - The Optical Shaft Encoder.
 - Used for VFO knobs & other controls in many modern radios.
 - Using 2 detectors allows the speed & direction of the rotation to be detected.




84



Optoelectronics

Photovoltaic Cells

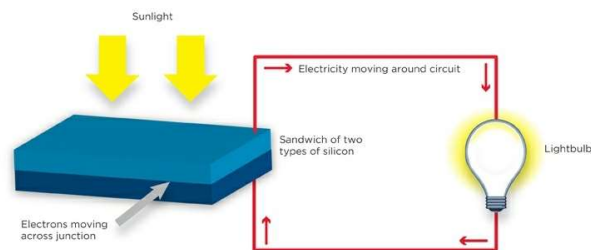- The photoconductive (a.k.a. – photoelectric) effect can be used in reverse to generate power.



85



Optoelectronics

Photovoltaic Cells

- If sufficient light falls on a P-N junction, free electrons in the N-type material will absorb energy & flow across the junction into the P-type material.
 - The most common material used is Silicon.
 - The most efficient material is Gallium-Arsenide.
 - The efficiency is the relative fraction of the light energy that is converted to electrical energy.
 - A fully-illuminated junction yields about 0.5 VDC.

86



Optoelectronics

Photovoltaic Cells

- Photovoltaic cells are rapidly becoming widely used for commercial power generation.



87

E6F01 -- What absorbs the energy from light falling on a photovoltaic cell?

- A. Protons
- B. Photons
- C. Electrons
- D. Holes

88

E6F02 -- What happens to the conductivity of a photoconductive material when light shines on it?

- A. It increases
- B. It decreases
- C. It stays the same
- D. It becomes unstable

89

E6F03 -- What is the most common configuration of an optoisolator or optocoupler?

- A. A lens and a photomultiplier
- B. A frequency modulated helium-neon laser
- C. An amplitude modulated helium-neon laser
- D. An LED and a phototransistor

90

E6F04 -- What is the photovoltaic effect?

- A. The conversion of voltage to current when exposed to light
- B. The conversion of light to electrical energy
- C. The conversion of electrical energy to mechanical energy
- D. The tendency of a battery to discharge when used outside

91

E6F05 -- Which describes an optical shaft encoder?

- A. A device which detects rotation of a control by interrupting a light source with a patterned wheel
- B. A device which measures the strength a beam of light using analog to digital conversion
- C. A digital encryption device often used to encrypt spacecraft control signals
- D. A device for generating RTTY signals by means of a rotating light source.

92

E6F06 -- Which of these materials is most commonly used to create photoconductive devices?

- A. A crystalline semiconductor
- B. An ordinary metal
- C. A heavy metal
- D. A liquid semiconductor

93

E6F07 -- What is a solid state relay?

- A. A relay using transistors to drive the relay coil
- B. A device that uses semiconductors to implement the functions of an electromechanical relay
- C. A mechanical relay that latches in the on or off state each time it is pulsed
- D. A semiconductor passive delay line

94

E6F08 -- Why are optoisolators often used in conjunction with solid state circuits when switching 120 VAC?

- A. Optoisolators provide a low impedance link between a control circuit and a power circuit
- B. Optoisolators provide impedance matching between the control circuit and power circuit
- C. Optoisolators provide a very high degree of electrical isolation between a control circuit and the circuit being switched
- D. Optoisolators eliminate the effects of reflected light in the control circuit

95

E6F09 -- What is the efficiency of a photovoltaic cell?

- A. The output RF power divided by the input DC power
- B. Cost per kilowatt-hour generated
- C. The open-circuit voltage divided by the short-circuit current under full illumination
- D. The relative fraction of light that is converted to current

96

E6F10 -- What is the most common type of photovoltaic cell used for electrical power generation?

- A. Selenium
- B. Silicon
- C. Cadmium Sulfide
- D. Copper oxide

97

E6F11 -- What is the approximate open-circuit voltage produced by a fully-illuminated silicon photovoltaic cell?

- A. 0.1 V
- B. 0.5 V
- C. 1.5 V
- D. 12 V

98



Digital Logic

Logic Basics

- There are 2 different types of digital logic circuits that we will be discussing:
 - Combinational logic.
 - The output state is determined by a combination of the current input states.
 - Sequential (or synchronous) logic.
 - The output state is determined by a combination of the current input states **and** the previous output state.

99



Digital Logic

Logic Basics

- Boolean Algebra.
 - Boolean algebra was introduced by George Boole in 1847 in his book *The Mathematical Analysis of Logic*.
 - The use of Boolean algebra is essential to the design and understanding of digital logic circuits.

100



Digital Logic

Logic Basics

- Boolean Algebra.
 - In Boolean algebra, variables have only 2 values.
 - 0 or 1.
 - False or True.
 - Off or On.
 - A “truth table” is used to show the resulting outputs with all possible combinations of inputs.



101



Digital Logic

Logic Basics

- One-input elements.

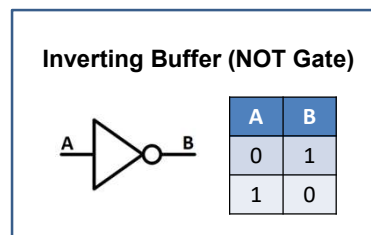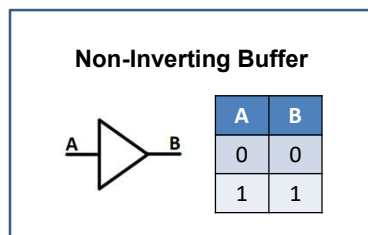


102



Digital Logic

Logic Basics

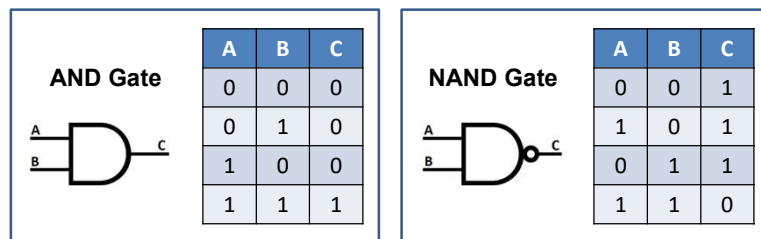- The AND/NAND operations.
 - The output is true/false only if ALL inputs are true.




103



Digital Logic

Logic Basics

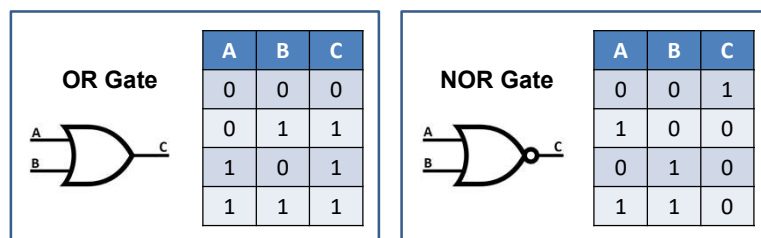- The OR/NOR operations.
 - The output is true/false if one or more of the inputs are true.





104



Digital Logic

Logic Basics

- The Exclusive OR (XOR/NOR) operations.
 - The output is true/false if one and only one of the inputs is true.

	XOR Gate	<table border="1"><thead><tr><th>A</th><th>B</th><th>C</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	0
	A	B	C														
	0	0	0														
	0	1	1														
	1	0	1														
1	1	0															
	<table border="1"><thead><tr><th>A</th><th>B</th><th>C</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	C	0	0	1	1	0	0	0	1	0	1	1	1	
A	B	C															
0	0	1															
1	0	0															
0	1	0															
1	1	1															
																	
	<table border="1"><thead><tr><th>A</th><th>B</th><th>C</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	C	0	0	1	1	0	0	0	1	0	1	1	1	
A	B	C															
0	0	1															
1	0	0															
0	1	0															
1	1	1															

105



Digital Logic

- Logic Basics
 - Positive & negative logic.
 - Positive logic.
 - True is represented by the highest voltage.
 - Negative logic.
 - True is represented by the lowest voltage.
 - A positive logic NAND gate is functionally equivalent to a negative logic NOR gate.
 - They have the same truth table.

106



Digital Logic

Logic Basics


- Tri-state logic allows multiple devices to be connected in parallel on same output bus.
 - Three output states.
 - Low (0).
 - High (1).
 - Off (high impedance).
 - Only one device can be “on” at a time.
 - All others MUST be in the high-impedance state.

107



Digital Logic

Tri-State Logic

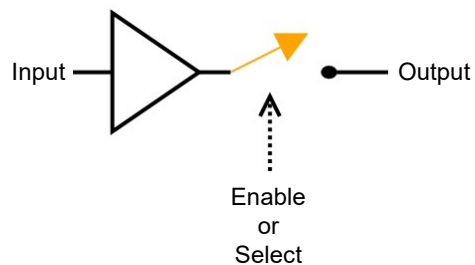

108

E6C03 -- What is tri-state logic?


- A. Logic devices with 0, 1, and high impedance output states
- B. Logic devices that utilize ternary math
- C. Low power logic devices designed to operate at 3 volts
- D. Proprietary logic devices manufactured by Tri-State Devices

109

E6C08 -- In Figure E6-3, what is the schematic symbol for a NAND gate?

- A. 1
- B. 2
- C. 3
- D. 4

Figure E6-3

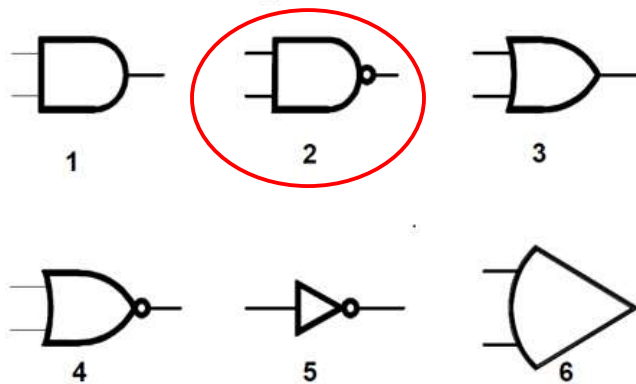


110

E6C10 -- In Figure E6-3, what is the schematic symbol for a NOR gate?

- A. 1
- B. 2
- C. 3
- D. 4

Figure E6-3

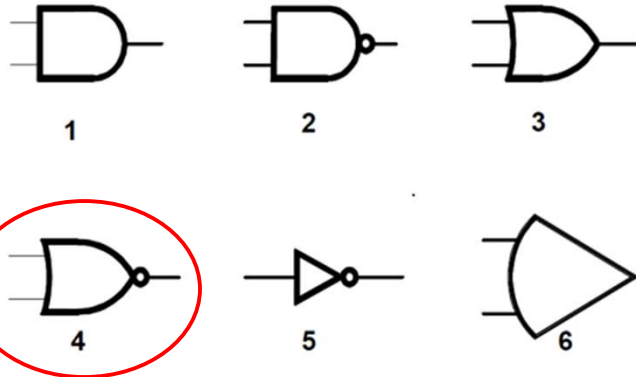


111

E6C11 -- In Figure E6-3, what is the schematic symbol for the NOT operation (inverter)?

- A. 2
- B. 4
- C. 5
- D. 6

Figure E6-3

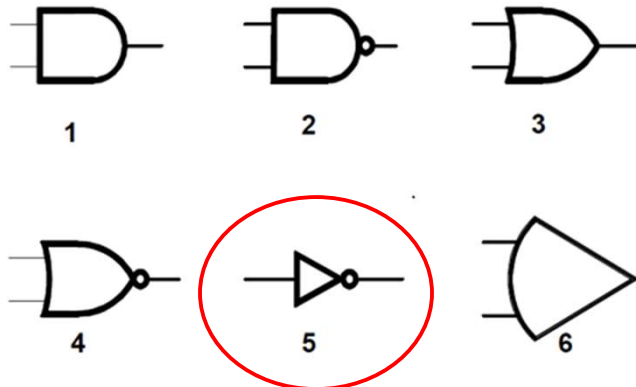

112

E7A07 -- What logical operation does a NAND gate perform?

- A. It produces logic 0 at its output only when all inputs are logic 0
- B. It produces logic 1 at its output only when all inputs are logic 1
- C. It produces logic 0 at its output if some but not all inputs are logic 1
- D. It produces logic 0 at its output only when all inputs are logic 1

113

E7A08 -- What logical operation does an OR gate perform?

- A. It produces logic 1 at its output if any or all inputs are logic 1
- B. It produces logic 0 at its output if all inputs are logic 1
- C. It only produces logic 0 at its output when all inputs are logic 1
- D. It produces logic 1 at its output if all inputs are logic 0

114

E7A09 -- What logical operation is performed by an exclusive NOR gate?

- A. It produces logic 0 at its output only if all inputs are logic 0
- B. It produces logic 1 at its output only if all inputs are logic 1
- C. It produces logic 0 at its output if only one input is logic 1
- D. It produces logic 1 at its output if only one input is logic 1

115

E7A10 -- What is a truth table?

- A. A table of logic symbols that indicate the high logic states of an op-amp
- B. A diagram showing logic states when the digital device output is true
- C. A list of inputs and corresponding outputs for a digital device
- D. A table of logic symbols that indicates the low logic states of an op-amp

116

E7A11 -- What is the name for logic which represents a logic "1" as a high voltage?

- A. Reverse Logic
- B. Assertive Logic
- C. Negative logic
- D. Positive Logic

117



Digital Logic

Sequential and Synchronous Logic

- The current output state is dependent on both the current input states and on the previous output states.
 - Must include some form of “memory”.

118



Digital Logic

Sequential and Synchronous Logic

- Flip-flops.
 - a.k.a -- Bi-stable multivibrator, latch.
 - A flip-flop has 2 stable states.
 - There are several different types of flip-flops.
 - S-R, J-K, D, T.
 - Gated, non-gated.
 - Clocked, non-clocked.
 - Can be used as frequency divider.
 - Each flip-flop divides by 2.

119



Digital Logic

Sequential and Synchronous Logic

- Synchronous and asynchronous flip-flops.
 - Synchronous flip-flops.
 - There is an additional input called the "clock" input.
 - The output state changes **ONLY** at time determined by the clock input.
 - Asynchronous flip-flops.
 - There is no clock input.
 - The output state changes whenever any input changes state.

120



Digital Logic

Sequential and Synchronous Logic

- Dynamic versus Static Inputs.
 - Dynamic inputs.
 - a.k.a. – Edge-triggered.
 - The flip-flop acts **ONLY** when the clock input changes state.
 - The flip-flop is positive edge triggered if the output changes state on the 0-to-1 transition of the clock pulse.
 - The flip-flop is positive edge triggered if the output changes state on the 0-to-1 transition of the clock pulse.
 - The flip-flop is negative edge triggered if the output changes state on the 1-to-0 transition of the clock pulse.

121



Digital Logic

Sequential and Synchronous Logic

- Dynamic versus Static Inputs.
 - Static inputs.
 - a.k.a. – Level-triggered.
 - The flip-flop changes state when any input changes state.

122




Digital Logic

Sequential and Synchronous Logic

- Set-Reset (SR) Latch
 - Most basic latch type.

S	R	Action
0	0	No change
0	1	Q = 0
1	0	Q = 1
1	1	Forbidden

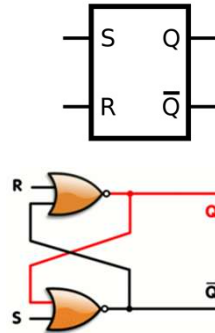


123



Digital Logic

Sequential and Synchronous Logic

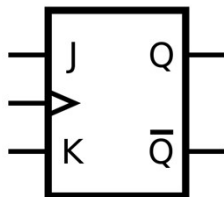- J-K flip-flop
 - Adds toggle function to SR latch.
 - Must be clocked.



Clock (>)	J	K	Action
0	--	--	No change
1	0	0	No change
1	0	1	Q = 0
1	1	0	Q = 1
1	1	1	Toggle (Q = not Q)


124



Digital Logic

Sequential and Synchronous Logic

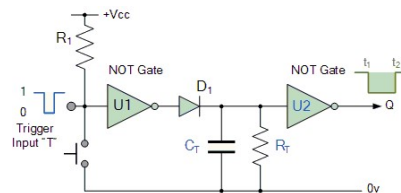- One-Shot or Monostable Multivibrator.
 - A one-shot generates one output pulse each time that a trigger pulse is received.
 - The length of the pulse is determined by the R-C time constant.




125



Digital Logic

Sequential and Synchronous Logic

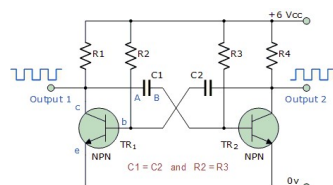- Astable multivibrator.
 - An astable multivibrator generates a series of pulses.
 - The digital equivalent of an oscillator.
 - The pulse length & the time between pulses are determined by R-C time constants.






126



Digital Logic

Sequential and Synchronous Logic

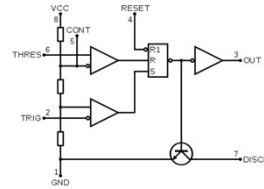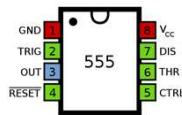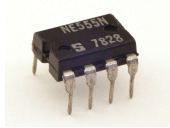- 555 Timer I.C.
 - One of the most popular ICs ever made.
 - ~1 billion/year.
 - Can be configured as either a monostable or as an astable multivibrator.




127



Digital Logic

Sequential and Synchronous Logic

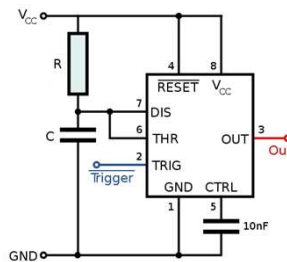- 555 Timer I.C.
 - Configured as a monostable multivibrator.
 - $T = 1.1 \times R \times C$




128



Digital Logic

Sequential and Synchronous Logic

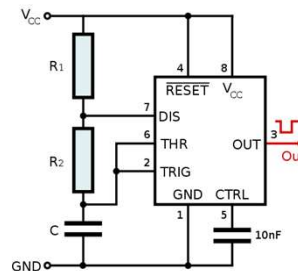- 555 Timer I.C.
 - Configured as an astable multivibrator
 - $f = \frac{1.46}{C1 \times (R1 + (2 \times R2))}$
 - The ratio of R1 to R2 determines the duty cycle.



129



Digital Logic

Sequential and Synchronous Logic


- Dividers and Counters.
 - Divide-by-N counter.
 - A series of flip-flops connected so that one output pulse occurs after every N input pulses.
 - Each flip-flop divides by 2.
 - Most counters provide an input to clear the count.
 - Counters can either count up or down.
 - A decade counter divides by 10.
 - A 4-stage counter (divide by 16) with feedback to reset counter to "0" after 10 input pulses.

130



Digital Logic

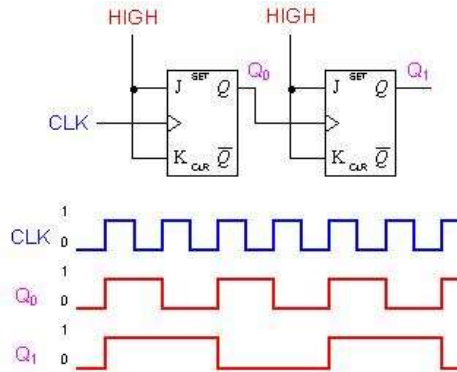- Sequential and Synchronous Logic
 - Frequency divider.
 - Cascaded J-K flip-flops.




131



Digital Logic

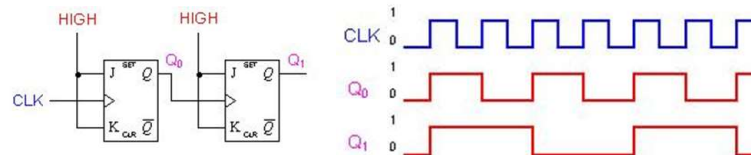- Sequential and Synchronous Logic
 - Frequency Dividers and Counters
 - Asynchronous (ripple) counter.
 - Each input pulse triggers the following stage, so the count "ripples" along the chain.




132



Digital Logic

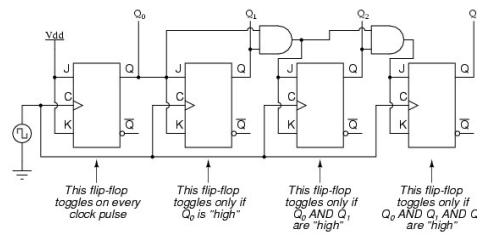- Sequential and Synchronous Logic
 - Frequency Dividers and Counters
 - Synchronous counter.
 - Each stage in counter triggered by common clock, so each stage in counter changes state at the same time.



133

E7A01 -- Which circuit is bistable?

- A. An AND gate
- B. An OR gate
- C. A flip-flop
- D. A bipolar amplifier

134

E7A02 -- What is the function of a decade counter?

- A. It produces one output pulse for every 10 input pulses
- B. It decodes a decimal number for display on a seven-segment LED display
- C. It produces 10 output pulses for every input pulse
- D. It decodes a binary number for display on a seven-segment LED display


135

E7A03 -- Which of the following can divide the frequency of a pulse train by 2?

- A. An XOR gate
- B. A flip-flop
- C. An OR gate
- D. A multiplexer


136

E7A04 -- How many flip-flops are required to divide a signal frequency by 4?

- A. 1
-  B. 2
- C. 4
- D. 8

137

E7A05 -- Which of the following is a circuit that continuously alternates between two states without an external clock?

- A. Monostable multivibrator
- B. J-K flip-flop
- C. T flip-flop
-  D. Astable multivibrator

138

E7A06 -- What is a characteristic of a monostable multivibrator?

- A. It switches momentarily to the opposite binary state and then returns to its original state after a set time
- B. It produces a continuous square wave oscillating between 1 and 0
- C. It stores one bit of data in either a 0 or 1 state
- D. It maintains a constant output voltage, regardless of variations in the input voltage

139



Digital Logic

Logic Families

- Several different technologies can be used to build digital circuits.
 - Vacuum tube.
 - RTL
 - ECL
 - TTL
 - CMOS
 - BiCMOS
- Tri-State Logic


140



Digital Logic

Logic Families (Ancient History)

- Vacuum tube.

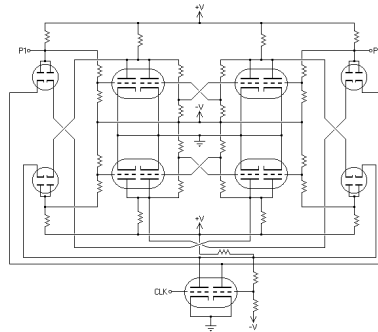


141



Digital Logic

Logic Families (Ancient History)

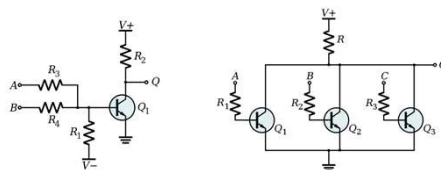- Resistor-Transistor-Logic (RTL).
 - The first IC digital logic family.
 - Introduced in 1961.
 - Used in the Apollo guidance system.
 - Quickly became obsolete & was replaced by TTL.




142



Digital Logic

Logic Families

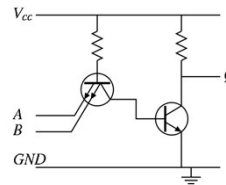- TTL Characteristics.
 - Transistor-Transistor-Logic.
 - Introduced in 1963 by Sylvania.
 - +5VDC supply voltage.
 - High level: >2.0 volts.
 - Low level: < 0.8 volts.
 - Threshold: ~0.7 volts.



143



Digital Logic

Logic Families


- TTL Characteristics.
 - Relatively high current consumption.
 - Relatively poor noise immunity.
 - ~1.2 volts.
 - Unconnected inputs are in a high logic state.
 - The best practice is to use pull-up or pull-down resistors on unused inputs.
 - A resistor tied to +5V to force a high voltage input state.
 - A resistor tied to 0V to force a low voltage input state.

144



Digital Logic

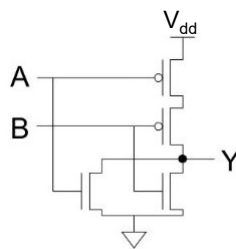- Logic Families
 - CMOS Characteristics.
 - Complementary Metal-Oxide Semiconductor.
 - Introduced by RCA in the late 1960s.




145



Digital Logic

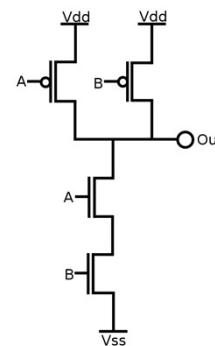- Logic Families
 - CMOS Characteristics.
 - 3-18 VDC supply voltage.
 - High level: $V_{dd} - 0.1$ volts.
 - Low level: $V_{ss} + 0.1$ volts.
 - Threshold: $\sim \frac{1}{2}$ supply voltage.
 - High noise immunity
 - $\sim V_{dd} - 0.2$ volts.
 - Sensitive to static damage.
 - Low power consumption.
 - A current pulse occurs during switchover.




146



Digital Logic

BiCMOS Logic

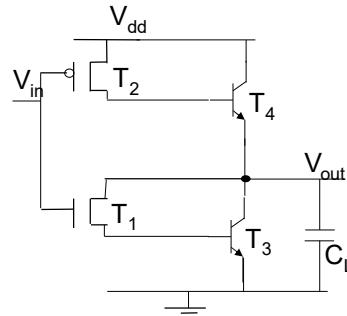- Both bipolar & CMOS devices on the same chip.
 - Has the high input impedance of CMOS.
 - Static-sensitive.
 - Has the low output impedance of bipolar.
 - Higher power consumption.
 - Complex manufacturing process.
 - More expensive.



147




Digital Logic

Programmable Logic

- Programmable Logic Device (PLD).
 - A programmable collection of logic gates and circuits in a single integrated circuit.
- Programmable Gate Array (PGA).
 - Complex logic functions can be created in a single integrated circuit.
- Field-Programmable Gate Array (FPGA).
 - The device can be programmed by the customer & not just by the manufacturer.


148

E6C04 -- Which of the following is an advantage of BiCMOS logic?

- A. Its simplicity results in much less expensive devices than standard CMOS
- B. It is immune to electrostatic damage
-  C. It has the high input impedance of CMOS and the low output impedance of bipolar transistors
- D. All these choices are correct

149

E6C05 -- What is an advantage of CMOS logic devices over TTL devices?

- A. Differential output capability
- B. Lower distortion
- C. Immune to damage from static discharge
-  D. Lower power consumption

150

E6C06 -- Why do CMOS digital integrated circuits have high immunity to noise on the input signal or power supply?

- A. Large bypass capacitance is inherent
- B. The input switching threshold is about two times the power supply voltage
- C. The input switching threshold is about one-half the power supply voltage
- D. Bandwidth is very limited

151

E6C07 -- What best describes a pull-up or pull-down resistor?

- A. A resistor in a keying circuit used to reduce key clicks
- B. A resistor connected to the positive or negative supply line used to establish a voltage when an input or output is an open circuit
- C. A resistor that ensures that an oscillator frequency does not drift
- D. A resistor connected to an op-amp output that prevents signals from exceeding the power supply voltage

152

E6C09 -- What is a Programmable Logic Device (PLD)?

- A. A logic circuit that can be modified during use
- B. A programmable collection of logic gates and circuits in a single integrated circuit
- C. Programmable equipment used for testing digital logic integrated circuits
- D. A type of transistor whose gain can be changed by digital logic circuits

153



Questions?



154



Amateur Extra Class

Next Week
Chapter 6 (Part 1)
Electronic Circuits