



# Chapter 6

## Electronic Circuits



## Amplifiers

- Any circuit that increases the strength of a signal – voltage, current, or power.
  - Input voltages from microvolts to hundreds of volts.
  - Output powers from billionths of a watt to thousands of watts.



## Amplifiers

- Definitions.
  - Driver: Circuit that supplies the input signal to the amplifier.
  - Load: Circuit that receives the amplifier's output signal.
  - Final Amplifier: Last amplifier stage in a transmitter.




## Amplifiers

- Amplifier Gain.
  - Ratio of output signal to input signal.
    - Voltage gain =  $V_{OUT} / V_{IN}$
    - Current gain =  $I_{OUT} / I_{IN}$
    - Power gain =  $P_{OUT} / P_{IN}$
  - Can be expressed as simple ratio.
    - e.g. – Voltage gain = 10
  - Can be expressed in decibels.
    - e.g. – Power gain = 10 dB



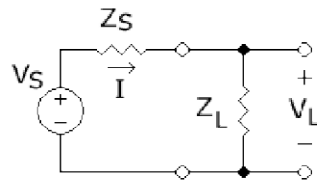
# Amplifiers

- Input and Output Impedances.
  - Input impedance is load seen by driver.
  - Output Impedance is source impedance.
  - Maximum power transfer occurs when the load impedance equals the source impedance.


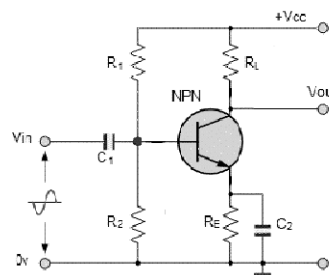
# Amplifiers


- Discrete Device Amplifiers
  - Common emitter.
    - Most common amplifier type.
    - Provides both voltage gain and current gain.
    - Input & output voltages 180° out of phase.
    - Fairly high input impedance.
    - Output impedance depends on  $R_L$ .





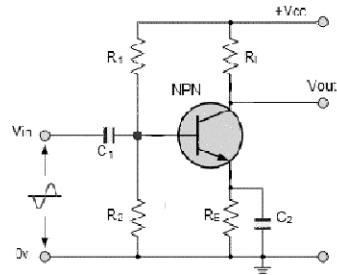
# Amplifiers

- Discrete Device Amplifiers
  - Common emitter.
    - $R_1$  &  $R_2$  provide fixed bias.
    - $R_E$  provides bias point stability.
      - a.k.a. – Self-bias.
      - Thermal runaway.
    - $C_2$  allows maximum AC signal gain.


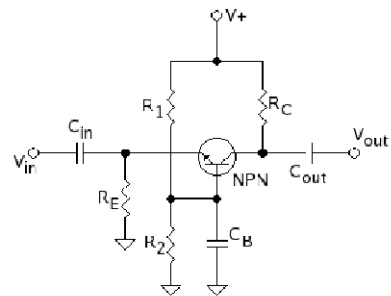
# Amplifiers



- Discrete Device Amplifiers
  - Common base.
    - Provides voltage gain.
    - Current gain  $< 1$ .
    - Input & output voltages in phase.
    - Low input impedance.
    - High output impedance.




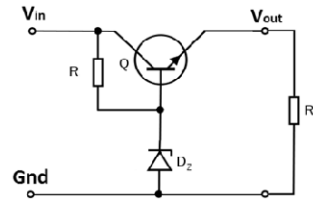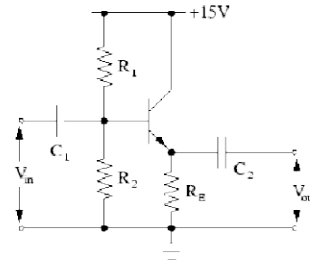
# Amplifiers


- Discrete Device Amplifiers
  - Common collector.
    - a.k.a. - Emitter follower.
    - Provides current gain.
    - Voltage gain  $< 1$ .
    - Input & output voltages in phase.
    - Fairly high input impedance.
    - Low output impedance.
    - Linear voltage regulator.



**E7B10 -- In Figure E7-1, what is the purpose of R1 and R2?**


- A. Load resistors
- ➔ B. Fixed bias
- C. Self bias
- D. Feedback

Figure E7-1

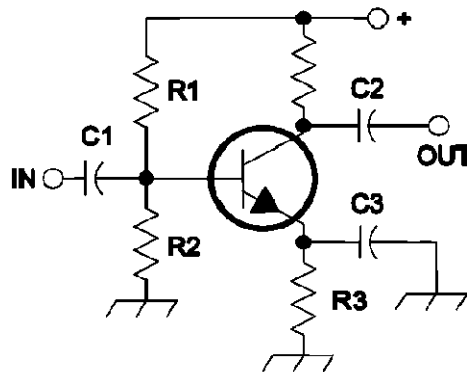


**E7B11 -- In Figure E7-1, what is the purpose of R3?**

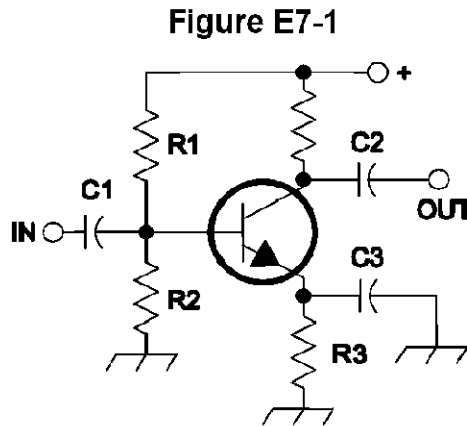- A. Fixed bias
- B. Emitter bypass
- C. Output load resistor
- D. Self bias




**E7B12 -- What type of amplifier circuit is shown in Figure E7-1?**

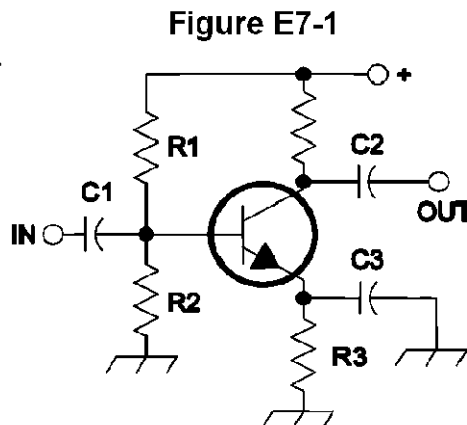- A. Common base
- B. Common collector
- C. Common emitter
- D. Emitter follower



**E7B13 -- In Figure E7-2, what is the purpose of R?**

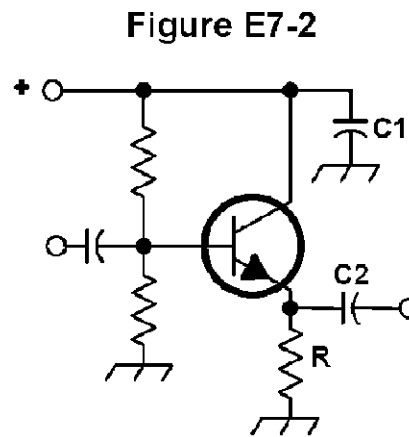- A. Emitter load
- B. Fixed bias
- C. Collector load
- D. Voltage regulation



**E7B15 -- What is one way to prevent thermal runaway in a bipolar transistor amplifier?**

- A. Neutralization
- B. Select transistors with high beta
- C. Use a resistor in series with the emitter
- D. All of these choices are correct




# Amplifiers

- Vacuum Tube Amplifiers
  - Each type of transistor amplifier circuit has a corresponding vacuum tube amplifier circuit.
    - Common-Emitter  $\leftrightarrow$  Common-Cathode.
    - Common-Base  $\leftrightarrow$  Grounded-Grid.
    - Common-Collector  $\leftrightarrow$  Common-Anode.
      - Emitter Follower  $\leftrightarrow$  Cathode Follower.


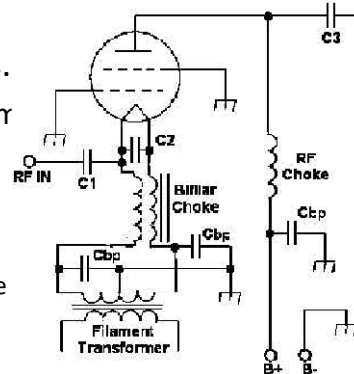
# Amplifiers

- Vacuum Tube Amplifiers.
  - Grounded-Grid Amplifiers.
    - Most common RF power amp
    - Stable.
      - Easier to neutralize.
    - Low input impedance.
      - Little or no input impedance






**E7B18 -- Which of the following is a characteristic of a grounded-grid amplifier?**

- A. High power gain
- B. High filament voltage
- C. Low input impedance
- D. Low bandwidth


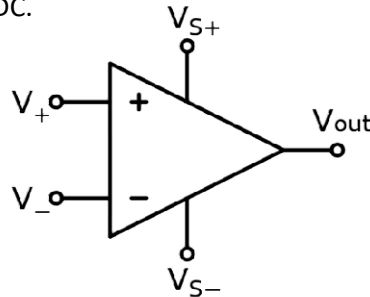
## Amplifiers


- Operational Amplifier (Op-Amp)
  - High-gain, direct-coupled, differential amplifier.
    - Differential input → Input signal is difference between inverting & non-inverting inputs.
    - Direct-coupled → Will amplify DC.
  - Ideal operational amplifier
    - Infinite input impedance.
    - Zero output impedance.
    - Infinite gain.
    - Flat frequency response.
    - Zero offset voltage.
      - $0 V_{IN} \rightarrow 0 V_{OUT}$





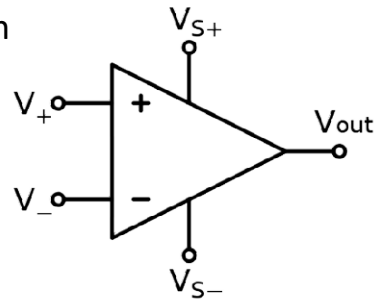
## Amplifiers

- Operational Amplifier (Op-Amp)
  - Circuit characteristics totally determined by external components.
  - In closed-loop configuration
    - Input voltage = 0.
    - Input current = 0.


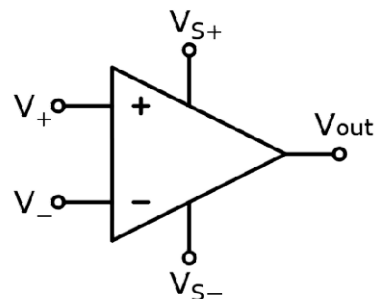
## Amplifiers



- Operational Amplifier (Op-Amp)
  - Operational amplifier specifications.
    - Open-loop gain.
    - Gain-Bandwidth.
    - Slew rate.
    - Input offset voltage.
      - Input voltage in closed-loop.
    - Input impedance.
    - Output impedance.





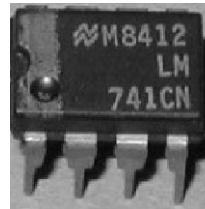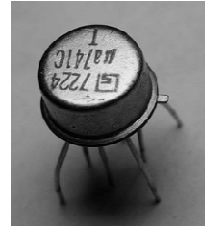
# Amplifiers

- Operational Amplifier (Op-Amp)
  - Practical operational amplifier.
    - Differential input.
    - Direct-coupled.
    - Very high input impedance.
    - Very low output impedance.
    - Very high voltage gain.
      - Up to 120 dB.
    - Wide bandwidth.


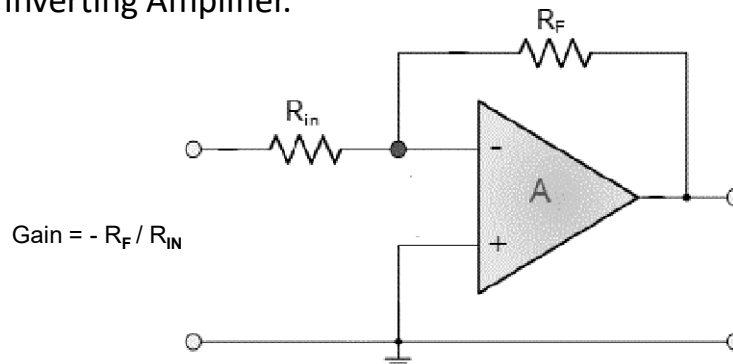
# Amplifiers

- Operational Amplifier (Op-Amp)
  - Inverting Amplifier.






## Amplifiers

- Operational Amplifier (Op-Amp)
  - Non-inverting Amplifier.

$$\text{Gain} = (R_F + R_2) / R_2$$

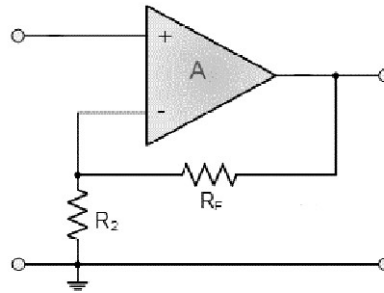

## Amplifiers


- Operational Amplifier (Op-Amp)
  - Differential Amplifier.

$$\text{Gain} = (R_3 + R_1) / R_1$$

or

$$\text{Gain} = (R_4 + R_2) / R_2$$


where:  $R_1 = R_2$  and  $R_3 = R_4$

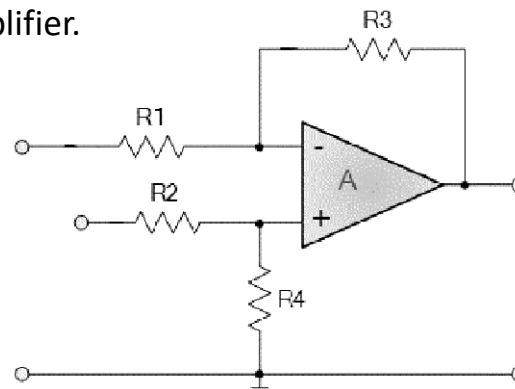



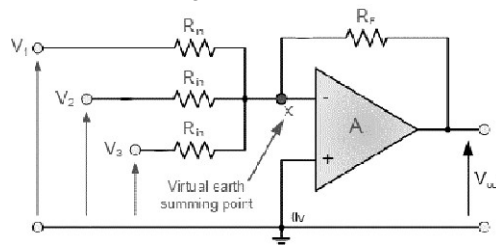
# Amplifiers

- Operational Amplifier (Op-Amp)
  - Summing Amplifier.
    - $V_{out} = -((V_1 \times R_F / R_{in}) + (V_2 \times R_F / R_{in}) + (V_3 \times R_F / R_{in}))$
    - $V_{out} = -(V_1 + V_2 + V_3) \times R_F / R_{in}$


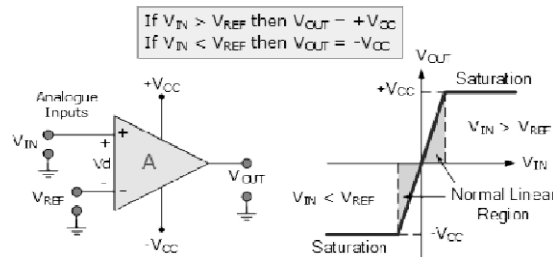
# Amplifiers

- Operational Amplifier (Op-Amp)
  - Voltage Comparator.
    - Compares 2 voltages.
    - Apply reference voltage to one input.






# Amplifiers

- Operational Amplifier (Op-Amp)
  - Voltage Comparator.
    - If input voltage is close to the threshold, minor variations (noise) can cause output to rapidly & randomly change between states.
      - This is called “chattering”.
    - Adding “hysteresis” eliminates chattering.
      - Output changes state slightly above the threshold on the way up & slightly below the threshold on the way down.


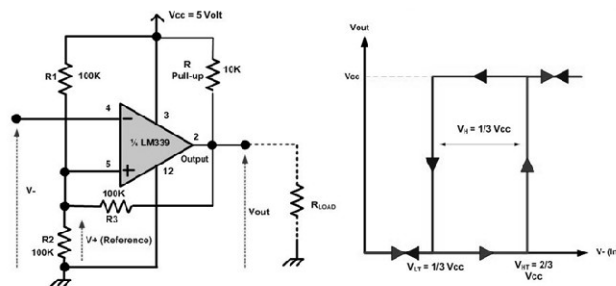
# Amplifiers

- Operational Amplifier (Op-Amp)
  - Voltage Comparator.
    - Adding feedback resistors provides hysteresis.



**E6C01 -- What is the function of hysteresis in a comparator?**

- ➔ A. To prevent input noise from causing unstable output signals
- B. To allow the comparator to be used with AC input signal
- C. To cause the output to change states continually
- D. To increase the sensitivity

**E6C02 -- What happens when the level of a comparator's input signal crosses the threshold?**

- A. The IC input can be damaged
- ➔ B. The comparator changes its output state
- C. The comparator enters latch-up
- D. The feedback loop becomes unstable

**E7G01 -- What is the typical output impedance of an integrated circuit op-amp?**

- A. Very low
- B. Very high
- C. 100 ohms
- D. 1000 ohms

**E7G03 -- What is the typical input impedance of an integrated circuit op-amp?**

- A. 100 ohms
- B. 1000 ohms
- C. Very low
- D. Very high




**E7G04 -- What is meant by the term op-amp input offset voltage?**

- A. The output voltage of the op-amp minus its input voltage
- B. The difference between the output voltage of the op-amp and the input voltage required in the immediately following stage
- C. The differential input voltage needed to bring the open-loop output voltage to zero
- D. The potential between the amplifier input terminals of the op-amp in an open-loop condition

**E7G07 -- What magnitude of voltage gain can be expected from the circuit in Figure E7-4 when R1 is 10 ohms and RF is 470 ohms?**

- A. 0.21
- B. 94
- C. 47
- D. 24

Figure E7-4

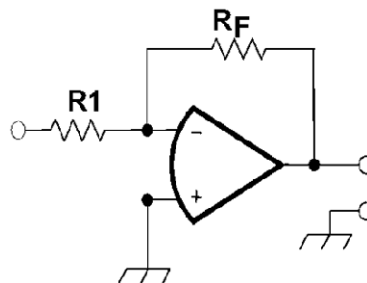


**E7G08 -- How does the gain of an ideal operational amplifier vary with frequency?**

- A. It increases linearly with increasing frequency
- B. It decreases linearly with increasing frequency
- C. It decreases logarithmically with increasing frequency
- D. It does not vary with frequency

**E7G09 -- What will be the output voltage of the circuit shown in Figure E7-4 if R1 is 1000 ohms, R<sub>F</sub> is 10,000 ohms, and 0.23 volts dc is applied to the input?**

- A. 0.23 volts
- B. 2.3 volts
- C. -0.23 volts
- D. -2.3 volts


Figure E7-4

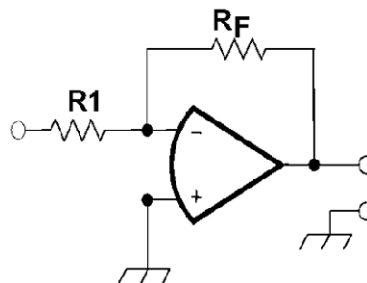

**E7G10 -- What absolute voltage gain can be expected from the circuit in Figure E7-4 when R1 is 1800 ohms and RF is 68 kilohms?**

- A. 1
- B. 0.03
- C. 38
- D. 76


Figure E7-4

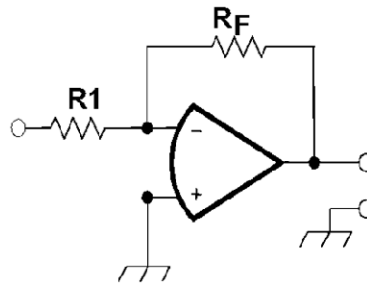

**E7G11 -- What absolute voltage gain can be expected from the circuit in Figure E7-4 when R1 is 3300 ohms and RF is 47 kilohms?**

- A. 28
- B. 14
- C. 7
- D. 0.07

Figure E7-4

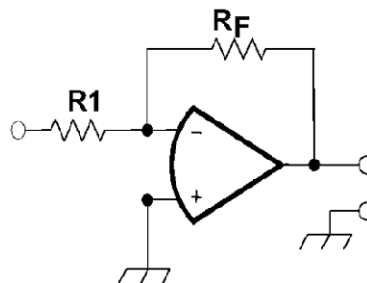


## E7G12 -- What is an integrated circuit operational amplifier?

- ➔ A. A high-gain, direct-coupled differential amplifier with very high input impedance and very low output impedance
- B. A digital audio amplifier whose characteristics are determined by components external to the amplifier
- C. An amplifier used to increase the average output of frequency modulated amateur signals to the legal limit
- D. A RF amplifier used in the UHF and microwave regions


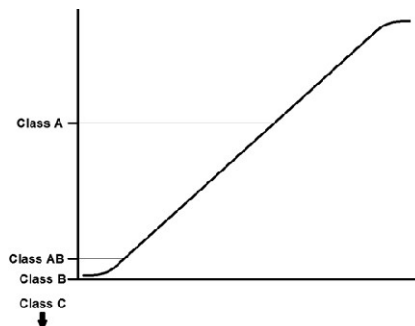
## Amplifiers


- Amplifier Load Line.
  - Output vs Input
    - Cutoff Region
    - Linear Region.
    - Saturation Region.





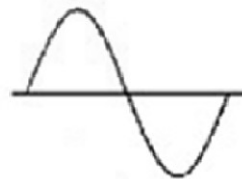
# Amplifiers

- Amplifier Classes.
  - Class A
    - On for 360°
    - Best linearity.
    - Least efficient. (25%-30%)


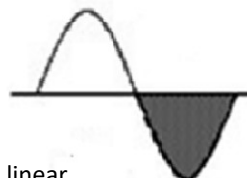
# Amplifiers

- Amplifier Classes.
  - Class B
    - On for 180°
    - Non-Linear (if AF).
      - 2 devices in push-pull configuration is linear.
    - Linear (if RF).
      - Flywheel action of tank circuit provides other half of cycle.
    - More efficient. (Up to 60%)






## Amplifiers

- Amplifier Classes.

- Class AB

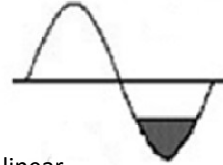- On for  $>180^\circ$  but  $<360^\circ$
    - Non-Linear (if AF).
      - 2 devices in push-pull configuration is linear.
    - Linear (if RF).
      - Flywheel action of tank circuit provides other half of cycle.
    - Compromise between classes A & B




## Amplifiers

- Amplifier Classes.

- Class C

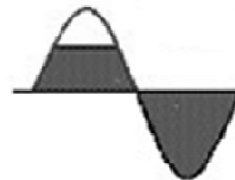
- On for  $<180^\circ$
    - Highly non-linear.
    - Most efficient. (Up to 80%)




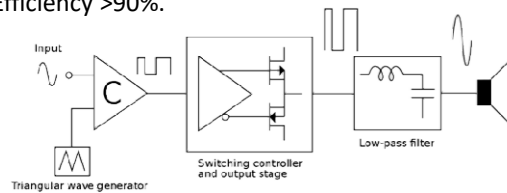
# Amplifiers

- Amplifier Classes.
  - Class D (Switching or Switch Mode)
    - Used for audio amplifiers.
    - Uses switching techniques to achieve high efficiency.
      - Switching speed well above highest frequency to be amplified.
      - Efficiency >90%.



# Amplifiers

- Distortion and Intermodulation.
  - Selecting amplifier class.
    - For audio, AM or SSB, a linear amplifier is required.
    - For CW or FM, a non-linear amplifier may be used.



## Amplifiers

- Distortion and Intermodulation.
  - Selecting amplifier class.
    - For best linearity & lowest efficiency, use Class A.
      - Low-level stages.
    - For a good compromise between linearity & efficiency, use Class AB.
      - Power amplifiers.



## Amplifiers



- Distortion and Intermodulation.
  - Selecting amplifier class.
    - For highest efficiency or intentional harmonics, use Class C.
      - Frequency multiplier stages.
      - CW transmitters.
      - FM transmitters & receivers.




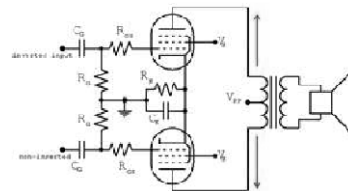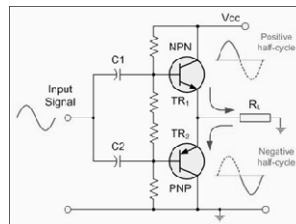
# Amplifiers

- Distortion and Intermodulation.
  - Selecting amplifier class.
    - Class B push-pull circuits.
      - Audio power amplifiers.
      - Even harmonics are reduced.



# Amplifiers

- Distortion and Intermodulation.
  - Distortion
    - Non-linearity results in distortion.
    - ALL physical components have non-linearity.
    - Distortion results in harmonics.
    - Can have low distortion or high efficiency, but not both.



## Amplifiers

- Distortion and Intermodulation.
  - Intermodulation.
    - 2 or more signals mixing together to produce other frequencies.
      - $F_{IMD} = (A \times F_1) \pm (B \times F_2)$ .
      - If A+B is odd, then odd-order intermodulation product.
        - $F_{imd}$  is near fundamental or odd harmonics of  $F_1$  &  $F_2$ .
      - If A+B is even then even-order intermodulation product.
        - $F_{imd}$  is near even harmonics of  $F_1$  &  $F_2$ .
    - Since odd-order IMD products are close to desired frequency, spurious signals can be transmitted.



## Amplifiers

- Distortion and Intermodulation.
  - Tuned amplifiers.
    - Power amplifiers are a compromise between linearity & efficiency.
    - Tuned output circuit acts like a “flywheel”, minimizing effects of distortion.
      - Single-ended class B & AB amplifiers.

**E7B01 -- For what portion of a signal cycle does a Class AB amplifier operate?**

- ➔ A. More than 180 degrees but less than 360 degrees
- B. Exactly 180 degrees
- C. The entire cycle
- D. Less than 180 degrees

**E7B02 -- What is a Class D amplifier?**

- ➔ A. A type of amplifier that uses switching technology to achieve high efficiency
- B. A low power amplifier using a differential amplifier for improved linearity
- C. An amplifier using drift-mode FETs for high efficiency
- D. A frequency doubling amplifier

**E7B03 -- Which of the following forms the output of a class D amplifier circuit?**

- ➔ A. A low-pass filter to remove switching signal components
- B. A high-pass filter to compensate for low gain at low frequencies
- C. A matched load resistor to prevent damage by switching transients
- D. A temperature compensating load resistor to improve linearity

**E7B04 -- Where on the load line of a Class A common emitter amplifier would bias normally be set?**

- ➔ A. Approximately half-way between saturation and cutoff
- B. Where the load line intersects the voltage axis
- C. At a point where the bias resistor equals the load resistor
- D. At a point where the load line intersects the zero bias current curve

**E7B06 -- Which of the following amplifier types reduces or eliminates even-order harmonics?**

- A. Push-push
- B. Push-pull
- C. Class C
- D. Class AB

**E7B07 -- Which of the following is a likely result when a Class C amplifier is used to amplify a single-sideband phone signal?**

- A. Reduced intermodulation products
- B. Increased overall intelligibility
- C. Signal inversion
- D. Signal distortion and excessive bandwidth

**E7B14 -- Why are switching amplifiers more efficient than linear amplifiers?**

- A. Switching amplifiers operate at higher voltages
- ➔ B. The power transistor is at saturation or cut off most of the time, resulting in low power dissipation
- C. Linear amplifiers have high gain resulting in higher harmonic content
- D. Switching amplifiers use push-pull circuits

**E7B16 -- What is the effect of intermodulation products in a linear power amplifier?**

- ➔ A. Transmission of spurious signals
- B. Creation of parasitic oscillations
- C. Low efficiency
- D. All of these choices are correct

**E7B17 -- Why are odd-order rather than even-order intermodulation distortion products of concern in linear power amplifiers?**

- ➔ A. Because they are relatively close in frequency to the desired signal
- B. Because they are relatively far in frequency from the desired signal
- C. Because they invert the sidebands causing distortion
- D. Because they maintain the sidebands, thus causing multiple duplicate signals



## Amplifiers

- Instability and Parasitic Oscillation.
  - Amplifier stability.
    - Excessive gain or undesired positive feedback can cause an amplifier to oscillate.
    - Can occur in any amplifier stage, not just power amplifiers.
    - Can result in:
      - Increased noise figure in receiver.
      - Spurious radiations.
      - Excessive heating.




## Amplifiers

- Instability and Parasitic Oscillation.
  - Neutralization.
    - Inter-electrode capacitances in amplifying device and/or stray capacitances in associated circuitry can cause an amplifier to oscillate at the frequency of operation.
    - Oscillation can be prevented by “neutralizing” the amplifier.
      - Feed small amount of signal back to input out-of-phase.


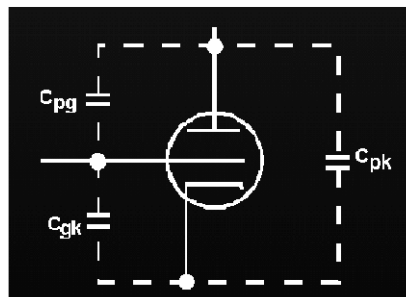
## Amplifiers

- Instability and Parasitic Oscillation.
  - Neutralization.








## Amplifiers

- Instability and Parasitic Oscillation.
  - Parasitic oscillation.
    - Not related to operating frequency.
    - Caused by resonances in surrounding circuitry.
    - Typically at VHF or UHF frequencies.
    - Parasitic oscillations in HF vacuum tube amplifiers are eliminated by adding parasitic suppressors to the plate or grid leads.
      - Coil in parallel with resistor.


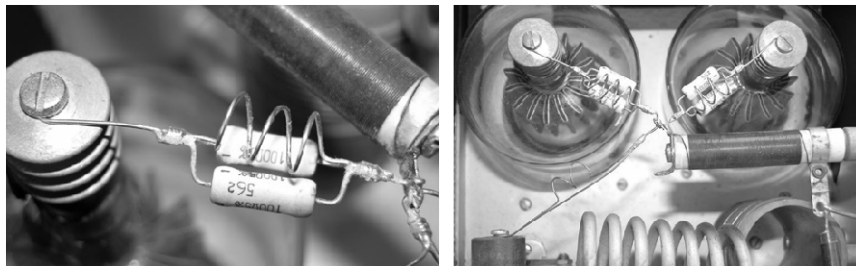
## Amplifiers

- Instability and Parasitic Oscillation.
  - Parasitic suppressor.





## Amplifiers

- Instability and Parasitic Oscillation.
  - Parasitic suppressor.



**E7B05 -- What can be done to prevent unwanted oscillations in an RF power amplifier?**

- A. Tune the stage for maximum SWR
- B. Tune both the input and output for maximum power
- C. Install parasitic suppressors and/or neutralize the stage
- D. Use a phase inverter in the output filter

**E7B08 -- How can an RF power amplifier be neutralized?**

- A. By increasing the driving power
- B. By reducing the driving power
- ➔ C. By feeding a 180-degree out-of-phase portion of the output back to the input
- D. By feeding an in-phase component of the output back to the input



## Signal Processing


- Oscillator Circuits & Characteristics.
  - Generates sine wave.
  - Amplifier with positive feedback.
    - $A_v$  = Amplifier voltage gain.
    - $\beta$  = Feedback ratio.
    - Loop Gain =  $A_v \times \beta$
    - If loop gain  $> 1$  and feedback signal is in phase, circuit will oscillate.
    - L-C circuit acts as a filter, restricting feedback to resonant frequency.



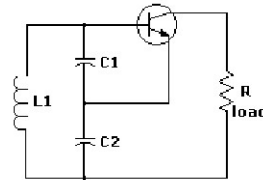
## Signal Processing

- Oscillator Circuits & Characteristics.

- Colpitts oscillator.
  - Tapped capacitance.



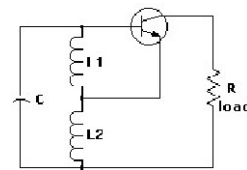
- Hartley oscillator.
  - Tapped inductance.


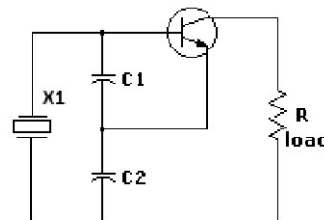
## Signal Processing

- Oscillator Circuits & Characteristics.

- Pierce oscillator.
  - Colpitts oscillator with inductor replaced with a quartz crystal.






## Signal Processing

- Oscillator Circuits & Characteristics.
  - Crystals.

- Equivalent circuit.

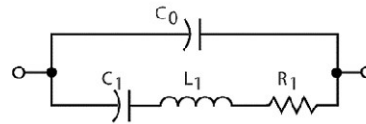- $C_1$  = Motional capacitance
    - $L_1$  = Motional inductance
    - $R_1$  = Loss resistance
    - $C_0$  = Electrode & stray capacitance



- Designed to operate with a specified parallel capacitance.



## Signal Processing

- Oscillator Circuits & Characteristics.

- Variable-frequency oscillator.

- Make either L or C adjustable.
      - Usually a Colpitts oscillator with adjustable capacitor.
    - Not as stable.



## Signal Processing

- Oscillator Circuits & Characteristics.
  - Oscillator stability.
    - Oscillator frequency can change with variations in power supply voltage, loading, temperature, and other factors.
    - Increased stability can be achieved by using:
      - GPS signals.
      - Rubidium oscillators.
      - Temperature-stabilized dielectric resonators.



## Signal Processing

- Oscillator Circuits & Characteristics
  - Microphonics & Thermal Drift.
    - Physical changes in the arrangement of the components of an oscillator can effect frequency.
      - Moving components changes stray capacitances.
      - Vibrations, such as the impact of sound waves, can cause changes in physical arrangement of components.
      - Effect is known as “microphonics”.
      - Reduce microphonics by mechanically isolating oscillator from rest of equipment.
        - Shock absorbers, etc.



## Signal Processing

- Oscillator Circuits & Characteristics
  - Microphonics & Thermal Drift.
    - Changes in ambient temperature can cause frequency to change.
      - Use components that are not susceptible to value changes with changes in temperature.
        - NPO capacitors, etc.
      - Provide oscillator (or crystal) with a non-changing temperature.
        - Crystal ovens.

### **E6D02 -- What is the equivalent circuit of a quartz crystal?**

- A. Motional capacitance, motional inductance, and loss resistance in series, all in parallel with a shunt capacitor representing electrode and stray capacitance
- B. Motional capacitance, motional inductance, loss resistance, and a capacitor representing electrode and stray capacitance all in parallel
- C. Motional capacitance, motional inductance, loss resistance, and a capacitor representing electrode and stray capacitance all in series
- D. Motional inductance and loss resistance in series, paralleled with motional capacitance and a capacitor representing electrode and stray capacitance

**E6E03 -- Which of the following is an aspect of the piezoelectric effect?**

- ➔ A. Mechanical deformation of material by the application of a voltage
- B. Mechanical deformation of material by the application of a magnetic field
- C. Generation of electrical energy in the presence of light
- D. Increased conductivity in the presence of light

**E7H01 -- What are three oscillator circuits used in Amateur Radio equipment?**

- A. Taft, Pierce and negative feedback
- B. Pierce, Fenner and Beane
- C. Taft, Hartley and Pierce
- ➔ D. Colpitts, Hartley and Pierce



**E7H02 -- Which describes a microphonic?**

- A. An IC used for amplifying microphone signals
- B. Distortion caused by RF pickup on the microphone cable
- C. Changes in oscillator frequency due to mechanical vibration
- D. Excess loading of the microphone by an oscillator

**E7H03 -- How is positive feedback supplied in a Hartley oscillator?**

- A. Through a tapped coil
- B. Through a capacitive divider
- C. Through link coupling
- D. Through a neutralizing capacitor

**E7H04 -- How is positive feedback supplied in a Colpitts oscillator?**

- A. Through a tapped coil
- B. Through link coupling
- C. Through a capacitive divider
- D. Through a neutralizing capacitor

**E7H05 -- How is positive feedback supplied in a Pierce oscillator?**

- A. Through a tapped coil
- B. Through link coupling
- C. Through a neutralizing capacitor
- D. Through a quartz crystal

**E7H06 -- Which of the following oscillator circuits are commonly used in VFOs?**

- A. Pierce and Zener
- ➔ B. Colpitts and Hartley
- C. Armstrong and deForest
- D. Negative feedback and balanced feedback

**E7H07 -- How can an oscillator's microphonic responses be reduced?**

- A. Use of NPO capacitors
- B. Eliminating noise on the oscillator's power supply
- C. Using the oscillator only for CW and digital signals
- ➔ D. Mechanically isolating the oscillator circuitry from its enclosure

**E7H08 -- Which of the following components can be used to reduce thermal drift in crystal oscillators?**

- ➔ A. NPO capacitors
- B. Toroidal inductors
- C. Wirewound resistors
- D. Non-inductive resistors

**E7H12 -- Which of the following must be done to insure that a crystal oscillator provides the frequency specified by the crystal manufacturer?**

- A. Provide the crystal with a specified parallel inductance
- ➔ B. Provide the crystal with a specified parallel capacitance
- C. Bias the crystal at a specified voltage
- D. Bias the crystal at a specified current

**E7H13 -- Which of the following is a technique for providing highly accurate and stable oscillators needed for microwave transmission and reception?**

- A. Use a GPS signal reference
- B. Use a rubidium stabilized reference oscillator
- C. Use a temperature-controlled high Q dielectric resonator

→ D. All of these choices are correct




## Signal Processing

- Frequency Synthesis
  - The use of frequency synthesis provides the capabilities of a variable frequency oscillator (VFO) but with the stability of a crystal oscillator (XO).
    - Virtually **ALL** modern equipment uses frequency synthesizers rather than VFO's to determine operating frequency.
  - Two primary types of frequency synthesizers:
    - Phase-locked loop (PLL).
    - Direct digital synthesis (DDS).


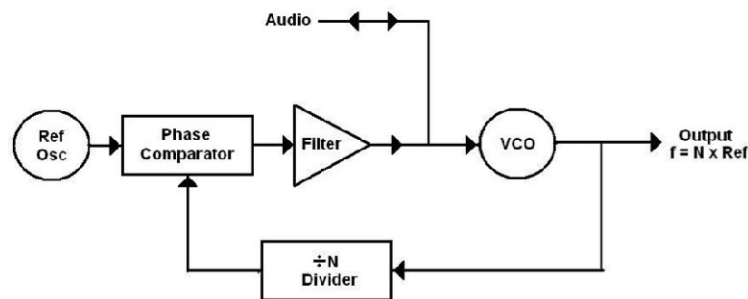
## Signal Processing

- Frequency Synthesis
  - Phase-Locked Loop (PLL).




## Signal Processing

- Frequency Synthesis
  - Phase-Locked Loop (PLL).
    - Servo loop
      - Error-detecting circuit with negative feedback.
    - Can do FM modulation & demodulation.
    - Capture range – Range of frequencies over which PLL can achieve lock.
    - Spectral impurities are mainly broadband phase noise.
    - PLL has been replaced in modern designs by direct digital synthesis.


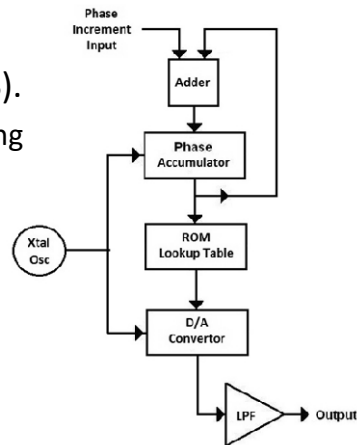
## Signal Processing

- Frequency Synthesis
  - Direct Digital Synthesis (DDS).
    - Generates sine wave by looking up values in a table.
    - Changing phase increment changes frequency.
    - Increase tuning range by adding PLL.
    - No phase noise, but spurs at discrete frequencies.



**E7H09 -- What type of frequency synthesizer circuit uses a phase accumulator, lookup table, digital to analog converter and a low-pass anti-alias filter?**

- A. A direct digital synthesizer
- B. A hybrid synthesizer
- C. A phase locked loop synthesizer
- D. A diode-switching matrix synthesizer

**E7H10 -- What information is contained in the lookup table of a direct digital frequency synthesizer?**

- A. The phase relationship between a reference oscillator and the output waveform
- B. The amplitude values that represent a sine-wave output
- C. The phase relationship between a voltage-controlled oscillator and the output waveform
- D. The synthesizer frequency limits and frequency values stored in the radio memories

**E7H11 -- What are the major spectral impurity components of direct digital synthesizers?**

- A. Broadband noise
- B. Digital conversion noise
- C. Spurious signals at discrete frequencies
- D. Nyquist limit noise



**E7H14 -- What is a phase-locked loop circuit?**

- A. An electronic servo loop consisting of a ratio detector, reactance modulator, and voltage-controlled oscillator
- B. An electronic circuit also known as a monostable multivibrator
- C. An electronic servo loop consisting of a phase detector, a low-pass filter, a voltage-controlled oscillator, and a stable reference oscillator
- D. An electronic circuit consisting of a precision push-pull amplifier with a differential input

**E7H15 -- Which of these functions can be performed by a phase-locked loop?**

- A. Wide-band AF and RF power amplification
- B. Comparison of two digital input signals, digital pulse counter
- C. Photovoltaic conversion, optical coupling
- D. Frequency synthesis, FM demodulation



## Signal Processing

- Mixers
  - Used to change the frequency of a signal.
  - Mathematically multiplies 2 frequencies together, generating 4 output frequencies.
    - $f_1 \times f_2 \rightarrow f_1, f_2, f_1+f_2, f_1-f_2$
  - Superheterodyne receiver.
    - $f_{RF} \times f_{LO} \rightarrow f_{LO} - f_{RF} = f_{IF}$




## Signal Processing

- Mixers
  - Only enough pre-amp gain should be used to overcome mixer losses.
  - Excessive input signal can:
    - Overload mixer circuit.
    - Distort signal.
    - Generate spurious mixer products.
  - Operation of a mixer is similar to operation of product detectors & modulators.



## Signal Processing

- Mixers

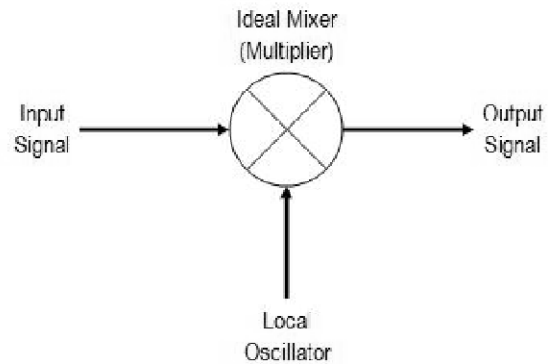

## Signal Processing


- Mixers

- Passive mixers.
  - Uses passive components such as diodes.
  - No amplification.
  - Some conversion loss.
  - Require strong LO signal.
  - Generate noise.




## Signal Processing

- Mixers
  - Single-balanced mixer.

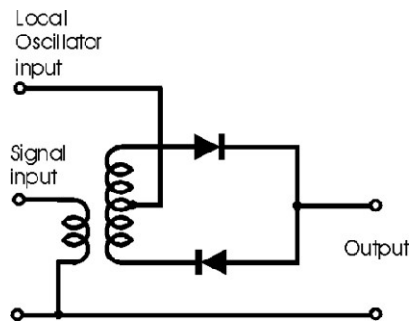
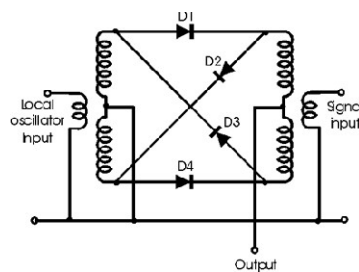
## Signal Processing

- Mixers
  - Double-balanced mixer.
    - $f_{RF}$  &  $f_{LO}$  are suppressed leaving only sum & difference frequencies.






## Signal Processing

- Mixers
  - Active mixers.
    - Uses active components such as transistors or FET's.
    - Amplification possible.
    - No conversion loss.
    - Less LO signal needed.
    - Generate less noise.
    - Strong signal handling capability not as good as passive mixers.



## Signal Processing

- Mixers
  - Dual-gate MOSFET mixer.

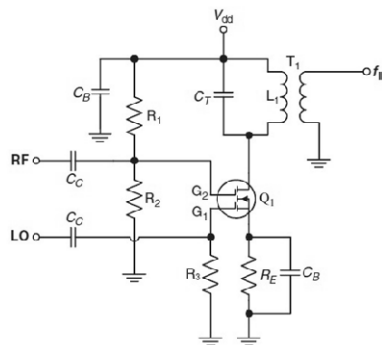

**E7E08 -- What are the principal frequencies that appear at the output of a mixer circuit?**

- A. Two and four times the original frequency
- B. The sum, difference and square root of the input frequencies
- C. The two input frequencies along with their sum and difference frequencies
- D. 1.414 and 0.707 times the input frequency

**E7E09 -- What occurs when an excessive amount of signal energy reaches a mixer circuit?**

- A. Spurious mixer products are generated
- B. Mixer blanking occurs
- C. Automatic limiting occurs
- D. A beat frequency is generated





## Signal Processing

- Modulation
  - Combining a modulating signal with an RF signal resulting in a signal that can be transmitted.
    - Modulating signal also known as the “baseband” signal.
    - Varying the amplitude of the signal is called amplitude modulation (AM).
    - Varying the frequency or phase of the signal is called angle modulation.
      - Frequency modulation (FM).
      - Phase modulation (PM).


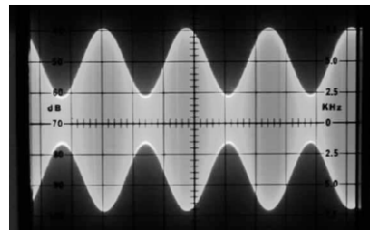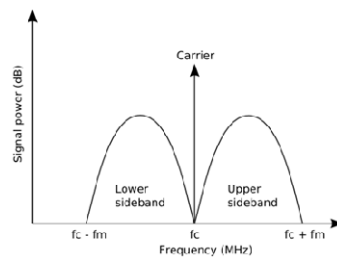
## Signal Processing

- Modulators
  - Amplitude modulation.
    - Multiplying (mixing) AF signal & carrier produces amplitude modulated signal.





## Signal Processing

- Modulators
  - Single-sideband modulation.
    - Filter method.
      - Start with AM double-sideband signal & use filters to remove one sideband & the carrier.
      - Better idea – use a balanced modulator (double-balanced mixer) to generate a double-sideband suppressed carrier signal. Then all you have to filter out is the unwanted sideband.



## Signal Processing


- Modulators
  - Single-sideband modulation.
    - Phasing (quadrature) method.
      - Generate 2 identical carrier signals,  $90^\circ$  out of phase.
      - Generate 2 identical audio signals,  $90^\circ$  out of phase.
      - Mix these together in a pair of balanced modulators & result is that the carrier & one sideband are canceled out leaving only one sideband.
      - $90^\circ$  phase shift of a band of audio frequencies difficult to accomplish in hardware, but relatively easy in software.
        - Hilbert-transform filters.
      - Most SDR transmitters use the phasing or quadrature method to generate SSB mathematically.




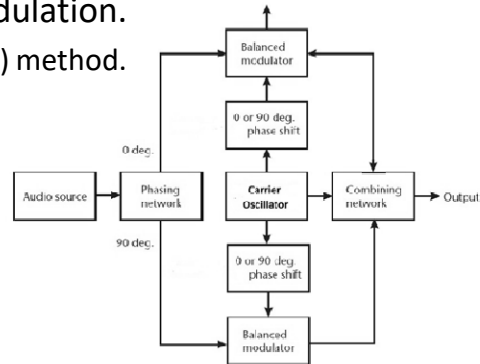
# Signal Processing

- Modulators
  - Single-sideband modulation.
    - Phasing (quadrature) method.



**E7E04 -- What is one way a single-sideband phone signal can be generated?**

- A. By using a balanced modulator followed by a filter
- B. By using a reactance modulator followed by a mixer
- C. By using a loop modulator followed by a mixer
- D. By driving a product detector with a DSB signal

**E7E07 -- What is meant by the term baseband in radio communications?**

- A. The lowest frequency band that the transmitter or receiver covers
- B. The frequency components present in the modulating signal
- C. The unmodulated bandwidth of the transmitted signal
- D. The basic oscillator frequency in an FM transmitter that is multiplied to increase the deviation and carrier frequency




## Signal Processing

- Modulators
  - Reactance Modulator.
    - A circuit that modulates a signal by varying the reactance of a circuit.
      - Usually by varying the bias voltage of a variable-capacitance diode (varicap).



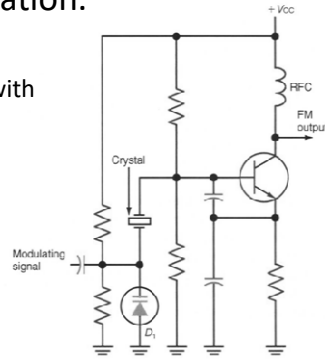
## Signal Processing

- Modulators
  - Frequency and phase modulation.
    - Direct FM
      - Frequency deviation constant with modulating frequency.
      - Generated by adding reactance modulator to oscillator circuit.


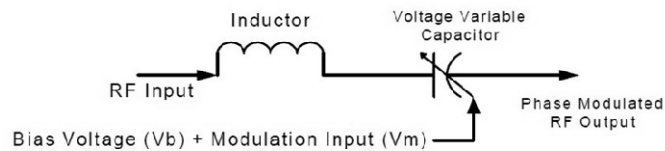
## Signal Processing

- Modulators
  - Frequency and phase modulation.
    - Indirect FM (phase modulation).
      - Frequency deviation increases with increasing modulating frequency.
      - Generated by adding reactance modulator to any stage other than the oscillator.





## Signal Processing

- Modulators
  - Pre-Emphasis and De-Emphasis.
    - With FM, deviation is constant regardless of modulating frequency.
    - With PM, deviation increases as modulating frequency increases.
    - In the transmitter, if we amplify the higher frequencies in the modulating signal more than the lower frequencies, we can make an FM signal “look like” a PM signal.
    - This is called “pre-emphasis”.



## Signal Processing

- Modulators
  - Pre-Emphasis and De-Emphasis.
    - In the receiver, if we attenuate the higher frequencies in the de-modulated signal with respect to the lower frequencies, we can make a received PM signal “look like” an FM signal.
    - This is called “de-emphasis”.



## Signal Processing

- Modulators
  - Pre-Emphasis and De-Emphasis.
    - Using pre-emphasis & de-emphasis yields a better signal-to-noise ratio.
    - A PM transmitter does not need pre-emphasis.
    - An FM receiver with de-emphasis can receive both FM & PM signals.

**E7E01 -- Which of the following can be used to generate FM phone emissions?**

- A. A balanced modulator on the audio amplifier
- ➔ B. A reactance modulator on the oscillator
- C. A reactance modulator on the final amplifier
- D. A balanced modulator on the oscillator

**E7E02 -- What is the function of a reactance modulator?**

- A. To produce PM signals by using an electrically variable resistance
- B. To produce AM signals by using an electrically variable inductance or capacitance
- C. To produce AM signals by using an electrically variable resistance
- D. To produce PM signals by using an electrically variable inductance or capacitance

**E7E03 -- How does an analog phase modulator function?**

- A. By varying the tuning of a microphone preamplifier to produce PM signals
- B. By varying the tuning of an amplifier tank circuit to produce AM signals
- C. By varying the tuning of an amplifier tank circuit to produce PM signals
- D. By varying the tuning of a microphone preamplifier to produce AM signals

**E7E05 -- What circuit is added to an FM transmitter to boost the higher audio frequencies?**

- A. A de-emphasis network
- B. A heterodyne suppressor
- C. An audio prescaler
- D. A pre-emphasis network

**E7E06 -- Why is de-emphasis commonly used in FM communications receivers?**

- A. For compatibility with transmitters using phase modulation
- B. To reduce impulse noise reception
- C. For higher efficiency
- D. To remove third-order distortion products





# Break


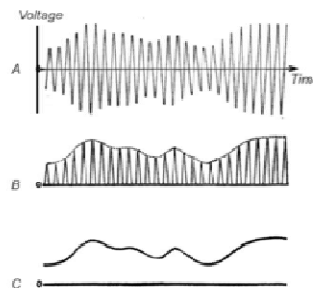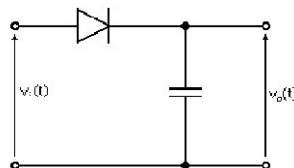
# Signal Processing

- Detectors and Demodulators
  - Detectors.
    - Simplest detector is the diode detector.
      - a.k.a. – Envelope detector.
      - Rectifies & filters RF signal.
      - Demodulates AM signals.







## Signal Processing

- Detectors and Demodulators
  - Product Detectors.
    - Actually, a mixer circuit.
    - Multiplies signal with a local oscillator to retrieve the modulating signal.
      - $f_{RF} \times f_{LO} \rightarrow f_{RF} - f_{LO} \rightarrow f_{AF}$
    - Local oscillator sometimes called a “beat frequency oscillator”.
      - Simulates the original carrier.
    - Demodulates AM, SSB. & CW signals.



## Signal Processing

- Detectors and Demodulators
  - Product Detectors.
    - For AM, local oscillator frequency & phase must precisely match AM signal carrier.
    - For SSB, local oscillator frequency must match carrier frequency of suppressed carrier.
    - For CW, local oscillator frequency is offset from signal frequency to produce a sidetone.




## Signal Processing

- Detectors and Demodulators
  - Direct Conversion.
    - Local oscillator is at the frequency of the received signal.
    - Requires very stable local oscillator.
    - Many software-defined radios (SDR) typically use a modified direct-conversion technique.
      - Signal is converted to a baseband AF signal for A-to-D conversion & processing.


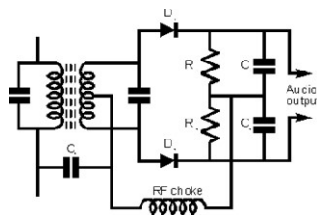
## Signal Processing


- Detectors and Demodulators
  - Detecting FM signals.
    - Frequency discriminator.
      - a.k.a. – Foster-Seeley Detector.





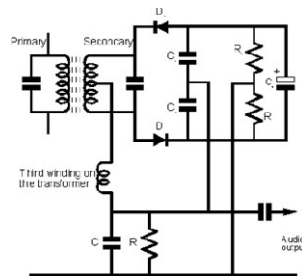
# Signal Processing

- Detectors and Demodulators
  - Detecting FM signals.
    - Ratio detector.


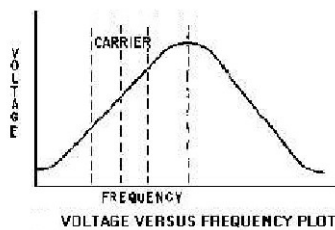
# Signal Processing

- Detectors and Demodulators
  - Detecting FM signals.
    - Slope detector.
      - Use AM receiver's selectivity curve to detect FM.



**E7E10 -- How does a diode detector function?**

- A. By rectification and filtering of RF signals
- B. By breakdown of the Zener voltage
- C. By mixing signals with noise in the transition region of the diode
- D. By sensing the change of reactance in the diode with respect to frequency

**E7E11 -- Which of the following type of detector is used for demodulating SSB signals?**

- A. Discriminator
- B. Phase detector
- C. Product detector
- D. Phase comparator

**E7E12 -- What is a frequency discriminator stage in a FM receiver?**

- A. An FM generator circuit
- B. A circuit for filtering two closely adjacent signals
- C. An automatic band-switching circuit
- D. A circuit for detecting FM signals



## **Digital Signal Processing (DSP) Software-Defined Radio (SDR)**

- Digital Signal Processing (DSP)
  - Part of virtually all modern transceivers.
  - Allows signal processing difficult or impossible to obtain by analog methods.
  - Digital signals can be regenerated (duplicated) many times without error.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Representation of Numbers.
    - Floating Point.
      - Similar to scientific notation.
      - Greater range of numbers can be handled.
      - Not necessary for DSP since range of numbers limited by precision of ADC.
      - Used in computers.
    - Fixed Point.
      - Fraction  $<1$ .
      - Used for most DSP in amateur equipment




## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Procedure:
    - Convert analog signal to series of numbers.
    - Process series of numbers mathematically.
    - Convert resulting series of numbers back to analog signal.


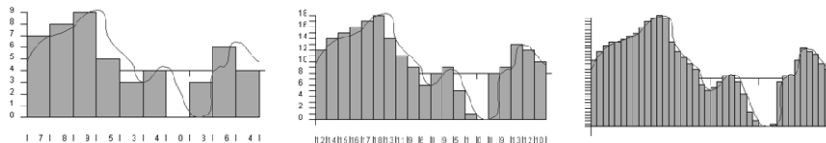
## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Analog-to-digital conversion.
    - Sequential sampling.
      - Sample signal at regular intervals (sequential sampling).
      - Convert signal value to a number.
      - Higher sampling rates yields higher accuracy.
      - More “bits” in the number yields higher accuracy



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Sine wave, alias sine wave, harmonic sampling.
    - If sample rate is less than frequency of signal being sampled, result does not match input signal.
      - Retains general shape of sine wave but at lower frequency.
      - Downward frequency translation can be useful.
      - Longer time between samples results in more processing time.




## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Sine wave, alias sine wave, harmonic sampling.
    - Harmonic sampling.
      - If frequency of signal being sampled is about twice the sampling rate, result is exactly same as if frequency is equal to sampling rate.
        - Must limit bandwidth of signal being sampled.


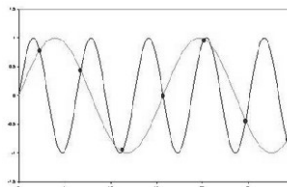
## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Sine wave, alias sine wave, harmonic sampling.
    - Aliasing.
      - Nyquist sampling theorem.
        - To avoid aliasing, sampling rate must be  $\geq 2x$  highest frequency being sampled.







## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Data converters.
    - Analog-to-digital converter (ADC).
      - Device that performs analog-to-digital conversion.
      - Produces a binary number that is directly proportional to value of the input voltage.
      - More bits in binary number → higher resolution.
        - 8 bits → 256 steps.
        - 10 bits → 1024 steps.
        - 16 bits → 65,536 steps.
        - 24 bits → 16,777,216 steps.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Data converters.
    - Analog-to-digital converter (ADC).
      - When used in an SDR receiver, the minimum detectable signal level (MDS) of the receiver is determined by:
        - Voltage corresponding to largest voltage (reference voltage).
        - Number of bits (sample width).






## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Data converters.
    - Analog-to-digital converter (ADC).
      - Dithering – Adding a small amount of noise to the input signal can improve


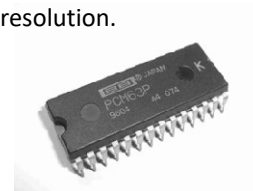
## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Data converters.
    - Digital-to-analog converter (DAC).
      - Device that performs digital-to-analog conversion.
      - Produces an output voltage that is directly proportional to value of a binary number.
      - More bits in binary number → higher resolution.
        - 8 bits → 256 steps.
        - 16 bits → 65,536 steps.
        - 24 bits → 16,777,216 steps.





## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Fourier Analysis and Fast Fourier Transform (FFT).
    - Fourier Analysis – Process of breaking a complex signal down into the individual frequencies that compose the signal.
      - e.g. – Fourier analysis of a square wave shows that it is composed of a fundamental frequency and all odd harmonics.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Fourier Analysis and Fast Fourier Transform (FFT).
    - Fourier Transform – A series of mathematical computations used to perform a Fourier analysis.
      - Mathematical equivalent of a spectrum analyzer.
        - Input is a signal in the time domain.
        - Output represents a signal in the frequency domain.
      - Requires a **LARGE** number of calculations.
      - FFT is a modern algorithm that reduces the number of calculations required by a factor of 100 or more.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Decimation and Interpolation.
    - DSP can perform functions impossible to do with analog circuitry.
      - e.g. – By using techniques called decimation & interpolation can shift the frequency of a signal by a non-integer amount.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Decimation and Interpolation.
    - Decimation – by removing samples, we can reduce the effective sample rate.
      - Decimation factor = ratio of input sampling rate to output sampling rate.
      - Must add an anti-aliasing filter to avoid interpreting high-frequency frequencies as lower frequency signals.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Decimation and Interpolation.
    - Interpolation – by adding samples, we can increase the effective sample rate.
      - Interpolation factor = ratio of input sampling rate to output sampling rate.
      - No anti-aliasing filter needed.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Decimation and Interpolation.
    - For example, to shift the sampling rate by  $\frac{3}{4}$ , we would:
      - Apply an interpolation factor of 3, then
      - Apply a decimation factor of 4

**E7F05 -- How frequently must an analog signal be sampled by an analog-to-digital converter so that the signal can be accurately reproduced?**

- A. At half the rate of the highest frequency component of the signal
- B. At twice the rate of the highest frequency component of the signal
- C. At the same rate as the highest frequency component of the signal
- D. At four times the rate of the highest frequency component of the signal

**E7F06 -- What is the minimum number of bits required for an analog-to-digital converter to sample a signal with a range of 1 volt at a resolution of 1 millivolt?**

- A. 4 bits
- B. 6 bits
- C. 8 bits
- D. 10 bits

**E7F07 -- What function can a Fast Fourier Transform perform?**

- A. Converting analog signals to digital form
- B. Converting digital signals to analog form
- C. Converting digital signals from the time domain to the frequency domain
- D. Converting 8-bit data to 16 bit data

**E7F08 -- What is the function of decimation with regard to digital filters?**

- A. Converting data to binary code decimal form
- B. Reducing the effective sample rate by removing samples
- C. Attenuating the signal
- D. Removing unnecessary significant digits

**E7F09 -- Why is an anti-aliasing digital filter required in a digital decimator?**

- ➔ A. It removes high-frequency signal components which would otherwise be reproduced as lower frequency components
- B. It peaks the response of the decimator, improving bandwidth
- C. It removes low frequency signal components to eliminate the need for DC restoration
- D. It notches out the sampling frequency to avoid sampling errors

**E7F11 -- What sets the minimum detectable signal level for an SDR in the absence of atmospheric or thermal noise?**

- A. Sample clock phase noise
- ➔ B. Reference voltage level and sample width in bits
- C. Data storage transfer rate
- D. Missing codes and jitter



**E7F16 -- How might the sampling rate of an existing digital signal be adjusted by a factor of  $\frac{3}{4}$ ?**

- A. Change the gain by a factor of  $\frac{3}{4}$
- B. Multiply each sample value by a factor of  $\frac{3}{4}$
- C. Add 3 to each input value and subtract 4 from each output value
- D. Interpolate by a factor of three, then decimate by a factor of four

**E8A01 -- What is the name of the process that shows that a square wave is made up of a sine wave plus all of its odd harmonics?**

- A. Fourier analysis
- B. Vector analysis
- C. Numerical analysis
- D. Differential analysis

**E8A04 -- What is "dither" with respect to analog to digital converters?**

- A. An abnormal condition where the converter cannot settle on a value to represent the signal
- B. A small amount of noise added to the input signal to allow more precise representation of a signal over time
- C. An error caused by irregular quantization step size
- D. A method of decimation by randomly skipping samples

**E8A09 -- How many levels can an analog-to-digital converter with 8 bit resolution encode?**

- A. 8
- B. 8 multiplied by the gain of the input amplifier
- C. 256 divided by the gain of the input amplifier
- D. 256

**E8A10 -- What is the purpose of a low pass filter used in conjunction with a digital-to-analog converter?**

- A. Lower the input bandwidth to increase the effective resolution
- B. Improve accuracy by removing out of sequence codes from the input
- C. Remove harmonics from the output caused by the discrete analog levels generated
- D. All of these choices are correct

**E8A11 -- What type of information can be conveyed using digital waveforms?**

- A. Human speech
- B. Video signals
- C. Data
- D. All of these choices are correct

**E8A12 -- What is an advantage of using digital signals instead of analog signals to convey the same information?**

- A. Less complex circuitry is required for digital signal generation and detection
- B. Digital signals always occupy a narrower bandwidth
- C. Digital signals can be regenerated multiple times without error
- D. All of these choices are correct

**E8A13 -- Which of these methods is commonly used to convert analog signals to digital signals?**

- A. Sequential sampling
- B. Harmonic regeneration
- C. Level shifting
- D. Phase reversal



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Software-Defined Radio (SDR) Systems
  - A software-defined radio (SDR) system is a radio communication system where components that have been typically implemented in hardware (e.g. mixers, filters, modulators/demodulators, detectors, etc.) are instead implemented by means of software on a computer or embedded computing devices.
  - Operation of radio can be changed simply by loading new software.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Software-Defined Radio (SDR) Systems
  - The ideal SDR receiver would be to attach an antenna to an analog-to-digital converter (ADC).
  - Similarly, the ideal SDR transmitter would be to attach a digital-to-analog converter (DAC) to an antenna.
  - Not feasible with current technology, so some compromise is necessary.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- Digital Signal Processing (DSP)
  - Software-Defined Radio (SDR).
    - Some analog processing still required.
    - Future is an all-digital radio.
    - Commercial SDR transceivers now available for amateur use.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)





## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- SDR Hardware
  - Early SDR designs for amateur radio used the following design concept:
    - A segment of RF spectrum is converted to an audio IF which is digitized & processed.
      - Can use lower speed A/D & D/A chips.
      - Possible to use the computer soundcard for the A/D & D/A functions.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- SDR Hardware
  - Current SDR designs for amateur radio use the following design concept:
    - A segment of the RF spectrum itself is digitized & processed.
      - Called "Direct Digital Conversion".
      - Requires high-speed A/D & D/A chips.
        - Direct conversion or flash conversion chips.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- SDR Hardware
  - Currently there are 4 types of SDR architecture:
    - Most processing is done in a computer, & the computer soundcard is used for A/D & D/A functions.
    - Most processing done in a computer, but the A/D & D/A functions are done in radio.
    - Most processing is done in the radio with a computer providing the user interface.
    - All processing done in the radio with conventional knobs & buttons for the user interface.



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- DSP Modulation
  - Any sinusoidal signal may be represented by adding a cosine (cos) wave and a sine (sin) wave.
    - The cosine wave is called the I (in-phase) signal.
    - The sine wave is called the Q (quadrature) signal.
  - For DSP it is convenient to consider the I & Q signals separately.
  - The I & Q signals can be represented mathematically as a complex number:
    - $X = I + jQ$





## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- DSP Modulation
  - Given the I & Q signals of the modulating waveform & 2 identical RF carriers 90° out of phase, **ANY** type of modulated signal can be generated.
    - AM
    - DSB
    - SSB
    - FM
    - PM



## Digital Signal Processing (DSP) Software-Defined Radio (SDR)

- DSP Modulation
  - Using I/Q modulation to generate a SSB signal is the mathematical equivalent of the quadrature method of SSB generation.
    - Generating an audio signal shifted by 90° requires a special type of DSP filter.
      - Hilbert transform filter.

**E7F01 -- What is meant by direct digital conversion as applied to software defined radios?**

- A. Software is converted from source code to object code during operation of the receiver
- B. Incoming RF is converted to a control voltage for a voltage controlled oscillator
- C. Incoming RF is digitized by an analog-to-digital converter without being mixed with a local oscillator signal
- D. A switching mixer is used to generate I and Q signals directly from the RF input

**E7F03 -- What type of digital signal processing filter is used to generate an SSB signal?**

- A. An adaptive filter
- B. A notch filter
- C. A Hilbert-transform filter
- D. An elliptical filter

**E7F04 -- What is a common method of generating an SSB signal using digital signal processing?**

- A. Mixing products are converted to voltages and subtracted by adder circuits
- B. A frequency synthesizer removes the unwanted sidebands
- C. Emulation of quartz crystal filter characteristics
- D. Combine signals with a quadrature phase relationship

**E7F10 -- What aspect of receiver analog-to-digital conversion determines the maximum receive bandwidth of a Direct Digital Conversion SDR?**

- A. Sample rate
- B. Sample width in bits
- C. Sample clock phase noise
- D. Processor latency

**E7F12 -- What digital process is applied to I and Q signals in order to recover the baseband modulation information?**

- A. Fast Fourier Transform
- B. Decimation
- C. Signal conditioning
- D. Quadrature mixing

**E7F17 -- What do the letters I and Q in I/Q Modulation represent?**

- A. Inactive and Quiescent
- B. Instantaneous and Quasi-stable
- C. Instantaneous and Quenched
- D. In-phase and Quadrature

**E8A08 -- Why would a direct or flash conversion analog-to-digital converter be useful for a software defined radio?**

- A. Very low power consumption decreases frequency drift
- B. Immunity to out of sequence coding reduces spurious responses
- C. Very high speed allows digitizing high frequencies
- D. All of these choices are correct



## **Filters and Impedance Matching**

- Filter Families and Response Types
  - Filters are circuits designed to pass certain frequencies and reject others.
    - R-C circuits.
    - R-L circuits.
    - R-L-C circuits.
  - A resonant circuit is a simple filter.
    - Most filters normally pass a wider range of frequencies than a simple resonant circuit.



## Filters and Impedance Matching

- Filter Families and Response Types
  - Passive filters.
    - Constructed using only passive components.
      - Capacitors.
      - Inductors.
      - Resistors.
    - Other types.
      - Crystal.
      - Mechanical.
      - Cavity.
  - Always have insertion loss.



## Filters and Impedance Matching

- Filter Families and Response Types
  - Cavity Filters
    - Cavity filters use the resonant properties of a conductive tube or box to act as a filter.
    - Cavity filters have an extremely narrow bandwidth (extremely high Q) and very low loss.
    - Cavity filters are often used in repeater duplexers.




## Filters and Impedance Matching

- Filter Families and Response Types
  - Active filters.
    - Include an amplifying device.
      - No insertion loss.
      - Can have gain.
    - Some type of filters can ONLY be built using active components.


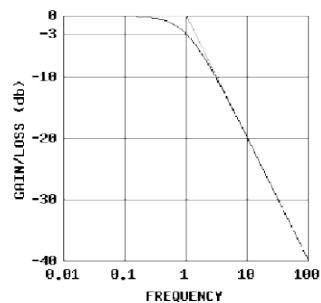
## Filters and Impedance Matching


- Filter Classification
  - Low-pass filter.
    - Passes all frequencies below the cut-off frequency.
    - Attenuates all frequencies above the cut-off frequency.
    - Cut-off frequency is the frequency where the response falls to 3 dB below the maximum level.





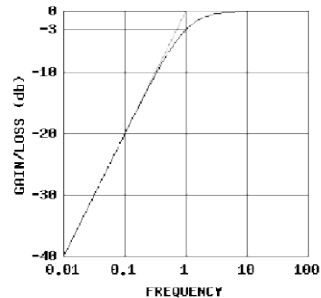
## Filters and Impedance Matching

- Filter Classification
  - High-pass filter.
    - Attenuates all frequencies below the cut-off frequency.
    - Passes all frequencies above the cut-off frequency.
    - Cut-off frequency is the frequency where the response rises to 3 dB below the maximum level.


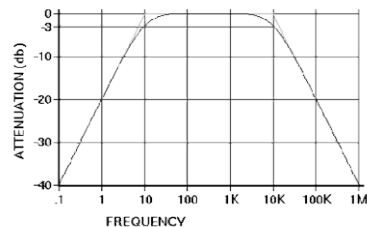
## Filters and Impedance Matching

- Filter Classification
  - Band-pass filter.
    - 2 cut-off frequencies.
      - Cut-off frequencies are frequencies where response is 3dB below maximum.
    - Passes all frequencies between the cut-off frequencies.
    - Attenuates all frequencies outside of the cut-off frequencies.







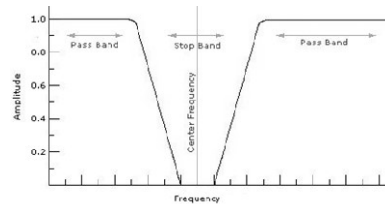
## Filters and Impedance Matching

- Filter Classification
  - Band-reject filter.
    - If the passband is narrow, it is called a notch filter.
    - 2 cut-off frequencies.
    - Attenuates all frequencies between the cut-off frequencies.
    - Passes all frequencies outside of the cut-off frequencies.



## Filters and Impedance Matching

- Filter Design
  - Definitions.
    - Response curve.
      - Output signal level vs. frequency.
      - Cut-off frequency = -3 dB point.
      - Cut-off transition.
        - Steepness of curve in transition region.
        - Steep transition curve → sharp filter.
    - Ripple.
      - Variations of response curve in passband or outside of passband.




## Filters and Impedance Matching

- Filter Design
  - Definitions.
    - Phase response.
      - Shift of signal phase vs. frequency.
      - Higher attenuation → more phase shift.
      - Linear phase shift means phase shift is smooth with no ripple as frequency changes.
      - Non-linear phase response can distort digital signals.
    - Ringing.
      - Oscillations continue after signal is removed.


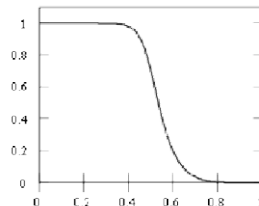
## Filters and Impedance Matching


- Filter Design
  - Butterworth
    - Minimum ripple in both pass band & stop band.
    - Cutoff transition smooth but not steep.
    - Smoothly varying phase response.





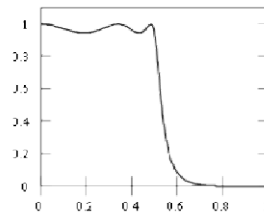
## Filters and Impedance Matching

- Filter Design
  - Chebyshev
    - Ripple in pass band.
    - Sharper cutoff transition.
    - Significant phase shift in pass band.


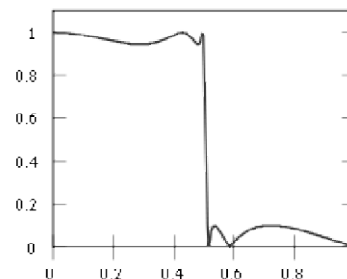
## Filters and Impedance Matching

- Filter Design
  - Elliptical
    - Ripple in both pass band & stop band.
    - Sharpest cutoff transition.
    - Notches are positioned at specific frequencies in stopband to make transition as sharp as possible.






## Filters and Impedance Matching

- Filter Design
  - Shape factor.
    - Measurement of “sharpness” of filter.
    - Ratio of -60dB bandwidth to -6dB bandwidth.
      - $SF = BW_{60dB} / BW_{6dB}$
    - The closer the ratio is to 1.0, the sharper the filter.
      - An ideal filter would have a shape factor of 1.0.



## Filters and Impedance Matching

- Filter Design
  - Shape factor.

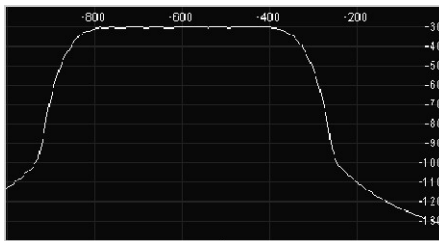


**Filter Characteristics**  
6dB Bandwidth 487 Hz,  
60dB Bandwidth 660 Hz  
Shape Factor ~1.36



## Filters and Impedance Matching

- Filter Design
  - Shape factor.

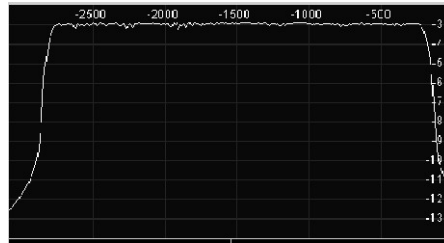

**Filter Characteristics**  
6dB Bandwidth 2587 Hz,  
60dB Bandwidth 2756 Hz  
Shape Factor ~1.06




## Filters and Impedance Matching

- Crystal filters.
  - IF stages of a receiver require very narrow bandwidth (high Q) filters with sharp transitions to filter out adjacent signals.
    - Cannot be achieved with L-C filters.
  - SSB transmitters require very narrow bandwidth (high Q) filters with sharp transitions to filter out unwanted sideband.
    - Cannot be achieved with L-C filters.



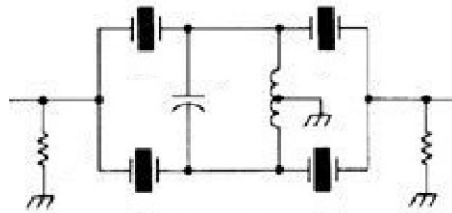
## Filters and Impedance Matching

- Crystal filters.
  - Lattice filter.
    - Typically used in SSB transmitters to remove unwanted sideband.


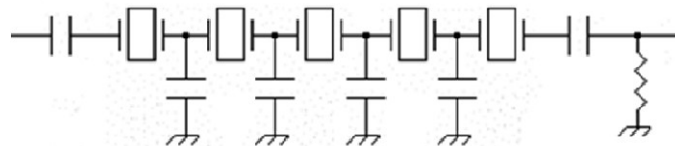
## Filters and Impedance Matching


- Crystal filters.
  - Ladder filter.
    - Bandwidth & response determined by frequencies of individual crystals.




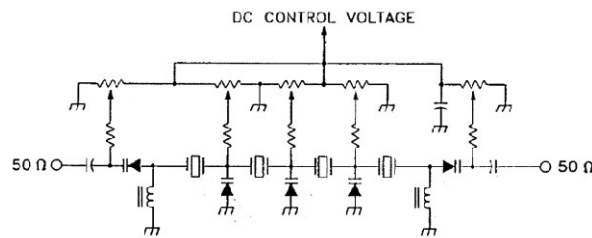
## Filters and Impedance Matching

- Crystal filters.
  - Jones filter.
    - Variable-bandwidth crystal ladder filter.
    - Invented by Lee J. Jones, WB4JTR, of Ten-Tec.



## Filters and Impedance Matching

- Crystal filters.
  - Jones filter.

**NOTE:** Both the book and the question pool (E7C09) mistakenly refer to the Jones filter as a crystal lattice filter when in fact, it is a crystal ladder filter.

**E7C05 -- Which filter type is described as having ripple in the passband and a sharp cutoff?**

- A. A Butterworth filter
- B. An active LC filter
- C. A passive op-amp filter
- D. A Chebyshev filter

**E7C06 -- What are the distinguishing features of an elliptical filter?**

- A. Gradual passband rolloff with minimal stop band ripple
- B. Extremely flat response over its pass band with gradually rounded stop band corners
- C. Extremely sharp cutoff with one or more notches in the stop band
- D. Gradual passband rolloff with extreme stop band ripple



**E7C07 -- What kind of filter would you use to attenuate an interfering carrier signal while receiving an SSB transmission?**

- A. A band-pass filter
- ➔ B. A notch filter
- C. A Pi-network filter
- D. An all-pass filter

**E7C08 -- Which of the following factors has the greatest effect in helping determine the bandwidth and response shape of a crystal ladder filter?**

- ➔ A. The relative frequencies of the individual crystals
- B. The DC voltage applied to the quartz crystal
- C. The gain of the RF stage preceding the filter
- D. The amplitude of the signals passing through the filter

**E7C09 -- What is a Jones filter as used as part of a HF receiver IF stage?**

- A. An automatic notch filter
- ➔ B. A variable bandwidth crystal lattice filter
- C. A special filter that emphasizes image responses
- D. A filter that removes impulse noise

**E7C10 -- Which of the following filters would be the best choice for use in a 2 meter repeater duplexer?**

- A. A crystal filter
- ➔ B. A cavity filter
- C. A DSP filter
- D. An L-C filter

**E7C14 -- Which mode is most affected by non-linear phase response in a receiver IF filter?**

- A. Meteor Scatter
- B. Single-Sideband voice
- C. Digital
- D. Video

**E7C15 -- What is a crystal lattice filter?**

- A. A power supply filter made with interlaced quartz crystals
- B. An audio filter made with four quartz crystals that resonate at 1-kHz intervals
- C. A filter with wide bandwidth and shallow skirts made using quartz crystals
- D. A filter with narrow bandwidth and steep skirts made using quartz crystals

**E7G02 -- What is the effect of ringing in a filter?**

- A. An echo caused by a long time delay
- B. A reduction in high frequency response
- C. Partial cancellation of the signal over a range of frequencies
- D. Undesired oscillations added to the desired signal




## Filters and Impedance Matching

- Active filters.
  - Active audio filters
    - Can be built without inductors.
    - Smaller & lighter.
    - No insertion loss & can have gain.
  - Op-amps.
    - Filter characteristics determined by external components.
    - Ringing can result if gain and/or Q are too high.
  - Best suited for audio filtering in receivers.


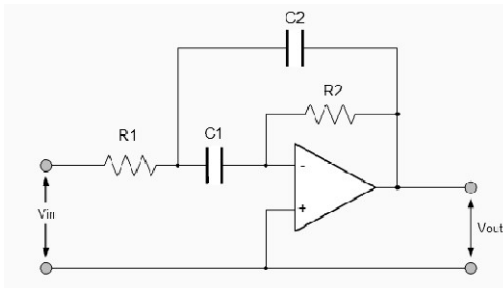
## Filters and Impedance Matching

- Active filters.
  - Active audio filters.
    - An active band-pass filter.



## Filters and Impedance Matching

- Active filters.
  - Active audio filters
    - Pick standard value capacitors.
      - Low-loss
      - Temperature stable.
      - Polystyrene (?)
    - Calculate resistors.

**E7G05 -- How can unwanted ringing and audio instability be prevented in a multi-section op-amp RC audio filter circuit?**

- ➔ A. Restrict both gain and Q
- B. Restrict gain, but increase Q
- C. Restrict Q, but increase gain
- D. Increase both gain and Q

**E7G06 -- Which of the following is the most appropriate use of an op-amp active filter?**

- A. As a high-pass filter used to block RFI at the input to receivers
- B. As a low-pass filter used between a transmitter and a transmission line
- C. For smoothing power-supply output
- ➔ D. As an audio filter in a receiver




## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - No tuning required.
  - No worry about selecting standard component values.
  - Adaptive processing.
    - Software can recognize & adapt to different signals & conditions to remove noise.
  - Requires computing hardware.


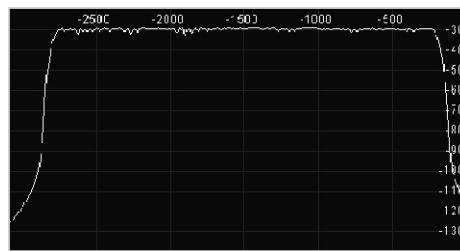
## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - Can build filters impossible to achieve with hardware.
    - “Brick wall” filters approach shape factors of 1.0.




**Filter Characteristics**  
6dB Bandwidth 2587 Hz,  
60dB Bandwidth 2756 Hz  
Shape Factor ~1.06



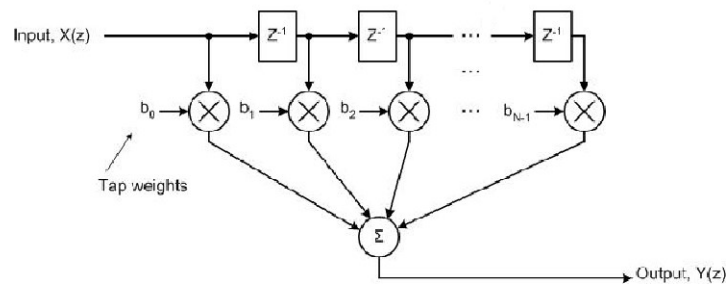
## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - Finite Impulse Response (FIR) filters.


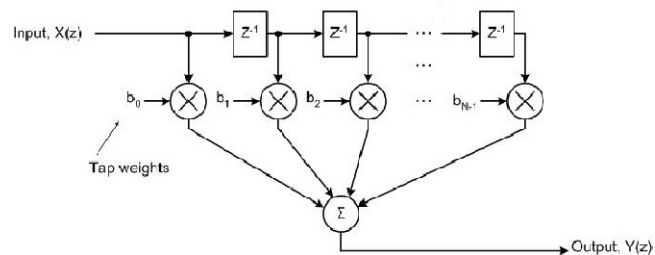
## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - Finite Impulse Response (FIR) filters.
    - Output ceases finite time after input is removed.








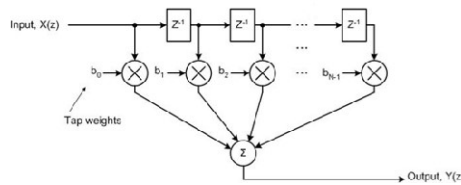
## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - Finite Impulse Response (FIR) filters.
    - Input is fed to a shift register.
      - Each stage in shift register is called a “tap”.
    - Input & outputs of each tap are scaled & added together to create the output signal.


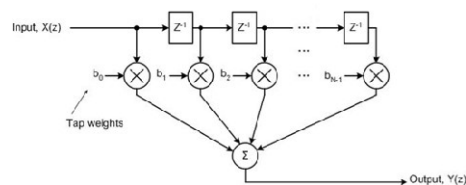
## Filters and Impedance Matching


- Digital Signal Processing (DSP) Filters.
  - Finite Impulse Response (FIR) filters.
    - Taps provide incremental signal delays used to create the filter function.
      - More taps → sharper filter.
      - More taps → longer delay.





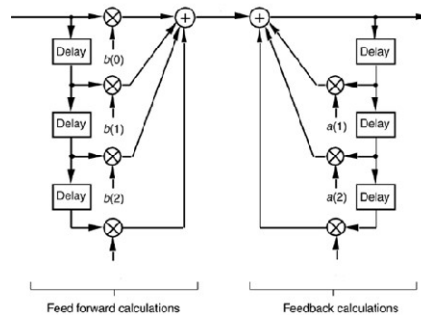
## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - Infinite Impulse Response (IIR) filters.


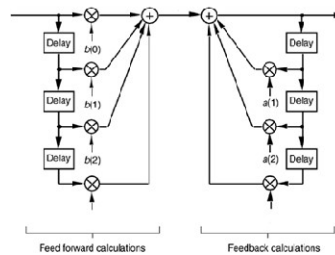
## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - Infinite Impulse Response (IIR) filters.
    - Output continues long after input is removed.
    - Feed-forward & feedback loops are used to create the filter function.





## Filters and Impedance Matching

- Digital Signal Processing (DSP) Filters.
  - FIR vs IIR filters.
    - FIR filters have linear phase response.
      - All frequency components are delayed by the same amount.  
**NOTE: Book is wrong!**
    - FIR filters are easier to design.
    - IIR filters require fewer software components.
      - Less computational power needed.

**E7F02 -- What kind of digital signal processing audio filter might be used to remove unwanted noise from a received SSB signal?**

- A. An adaptive filter
- B. A crystal-lattice filter
- C. A Hilbert-transform filter
- D. A phase-inverting filter

**E7F13 -- What is the function of taps in a digital signal processing filter?**

- A. To reduce excess signal pressure levels
- B. Provide access for debugging software
- C. Select the point at which baseband signals are generated
- D. Provide incremental signal delays for filter algorithms

**E7F14 -- Which of the following would allow a digital signal processing filter to create a sharper filter response?**

- A. Higher data rate
- B. More taps
- C. Complex phasor representations
- D. Double-precision math routines

**E7F15 -- Which of the following is an advantage of a Finite Impulse Response (FIR) filter vs an Infinite Impulse Response (IIR) digital filter?**

- A. FIR filters delay all frequency components of the signal by the same amount
- B. FIR filters are easier to implement for a given set of passband rolloff requirements
- C. FIR filters can respond faster to impulses
- D. All of these choices are correct




## **Filters and Impedance Matching**

- Impedance Matching.
  - If load & source impedances are not equal, an impedance matching network is needed for maximum power transfer.
  - Assuming a source impedance of  $50\Omega$ , the matching network must:
    - Cancel the reactive portion of the load impedance.
    - Transform the resistive component to  $50\Omega$ .


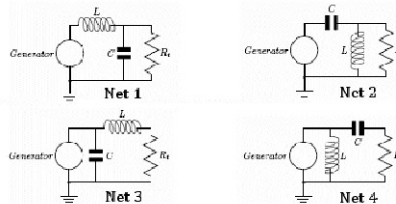
## Filters and Impedance Matching

- Impedance Matching.
  - L Networks.
    - Can match virtually any 2 impedances.
    - Q is fixed.
    - Usually only designed to work on a single band.




## Filters and Impedance Matching

- Impedance Matching.
  - Pi-Networks.
    - Equivalent to 2 L-networks connected back-to-back.
    - Matches wide range of load impedances.
    - Q can be varied depending on component values chosen.
    - Used in most tube amplifiers.



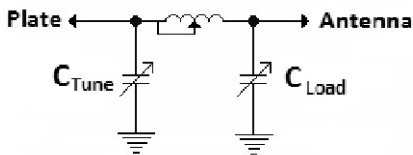
## Filters and Impedance Matching

- Impedance Matching.
  - Pi-Networks.
    - Adjust  $C_{\text{Tune}}$  for minimum plate current.
    - Adjust  $C_{\text{Load}}$  for maximum plate current.
    - Repeat until maximum power output is achieved **without** exceeding maximum tube plate current rating.


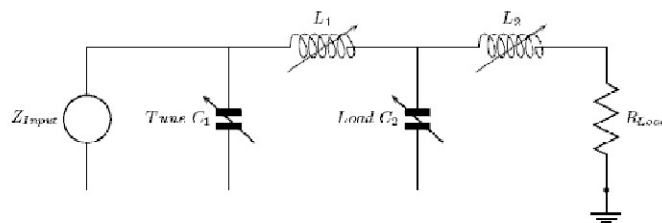
## Filters and Impedance Matching


- Impedance Matching.
  - Pi-L networks.
    - Add inductor to output of Pi network
    - More harmonic reduction.




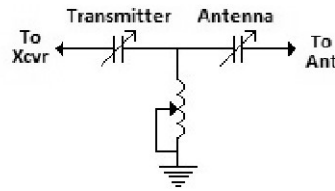
## Filters and Impedance Matching

- Impedance Matching.
  - T-Networks.
    - Can match wide range of impedances.
    - Lower loss than pi-network.
    - Used in most antenna tuners.
    - High-pass filter
      - Does **not** provide harmonic suppression.



**E7B09 -- Which of the following describes how the loading and tuning capacitors are to be adjusted when tuning a vacuum tube RF power amplifier that employs a pi-network output circuit?**

- A. The loading capacitor is set to maximum capacitance and the tuning capacitor is adjusted for minimum allowable plate current
- B. The tuning capacitor is set to maximum capacitance and the loading capacitor is adjusted for minimum plate permissible current
- C. The loading capacitor is adjusted to minimum plate current while alternately adjusting the tuning capacitor for maximum allowable plate current
- D. The tuning capacitor is adjusted for minimum plate current, while the loading capacitor is adjusted for maximum permissible plate current



**E7C01 -- How are the capacitors and inductors of a low-pass filter Pi-network arranged between the network's input and output?**

- A. Two inductors are in series between the input and output, and a capacitor is connected between the two inductors and ground
- B. Two capacitors are in series between the input and output and an inductor is connected between the two capacitors and ground
- C. An inductor is connected between the input and ground, another inductor is connected between the output and ground, and a capacitor is connected between the input and output
- D. A capacitor is connected between the input and ground, another capacitor is connected between the output and ground, and an inductor is connected between input and output

**E7C02 -- Which of the following is a property of a T-network with series capacitors and a parallel shunt inductor?**

- A. It is a low-pass filter
- B. It is a band-pass filter
- C. It is a high-pass filter
- D. It is a notch filter

**E7C03 -- What advantage does a Pi-L-network have over a Pi-network for impedance matching between the final amplifier of a vacuum-tube transmitter and an antenna?**

- ➔ A. Greater harmonic suppression
- B. Higher efficiency
- C. Lower losses
- D. Greater transformation range

**E7C04 -- How does an impedance-matching circuit transform a complex impedance to a resistive impedance?**

- A. It introduces negative resistance to cancel the resistive part of impedance
- B. It introduces transconductance to cancel the reactive part of impedance
- ➔ C. It cancels the reactive part of the impedance and changes the resistive part to a desired value
- D. Network resistances are substituted for load resistances and reactances are matched to the resistances

**E7C11 -- Which of the following is the common name for a filter network which is equivalent to two L networks connected back-to-back with the inductors in series and the capacitors in shunt at the input and output?**

- A. Pi-L
- B. Cascode
- C. Omega
- D. Pi

**E7C12 -- Which of the following describes a Pi-L network used for matching a vacuum-tube final amplifier to a 50-ohm unbalanced output?**

- A. A Phase Inverter Load network
- B. A Pi network with an additional series inductor on the output
- C. A network with only three discrete parts
- D. A matching network in which all components are isolated from ground



**E7C13 -- What is one advantage of a Pi-matching network over an L-matching network consisting of a single inductor and a single capacitor?**

- ➔ A. The Q of Pi networks can be varied depending on the component values chosen
- B. L networks can not perform impedance transformation
- C. Pi networks have fewer components
- D. Pi networks are designed for balanced input and output


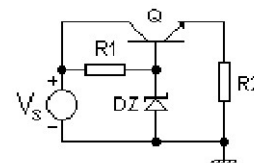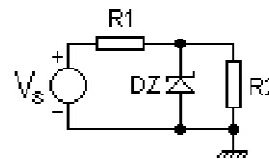
## Power Supplies

- Linear Voltage Regulators.
  - Shunt Regulators.
    - Lousy efficiency.
    - Constant current drawn from source.
    - Maximum current flows all the time.
  - Series Regulators.
    - Good efficiency.
    - Only the current required by the load flows.






## Power Supplies

- Linear Voltage Regulators.

- Basic series regulator circuit.

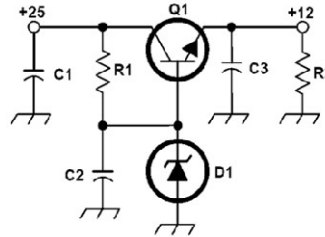- C1 -- Input by-pass capacitor.
      - Filters supply voltage.
    - C2 – Hum-filter capacitor.
      - Bypasses hum around D1.
    - C3 – Output by-pass capacitor.
      - Often 2 capacitors in parallel.
        - Large value capacitor to filter output.
        - Small value capacitor to prevent self-oscillation.




## Power Supplies

- Linear Voltage Regulators.

- Basic series regulator circuit.

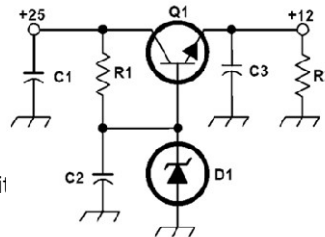
- D1 – Zener diode.
      - Provides voltage reference.
    - Q1 – Series pass transistor.
      - Increases current handling capability




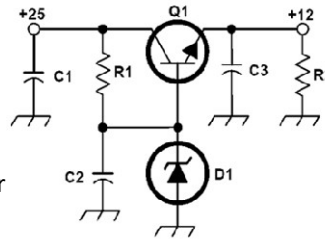
## Power Supplies

- Linear Voltage Regulators.
  - Basic series regulator circuit.
    - R1 – Bias resistor.
      - Provides bias current to D1 & Q1.
    - R2 – Load resistor.
      - Provides minimum load current for



## Power Supplies

- Linear Voltage Regulators.
  - IC “3-Terminal” Regulators.
    - Thermal shutdown.
    - Overvoltage protection.
    - Foldback current limiting.
    - LM78Lxx -- 100 mA.
    - LM78xx -- 1 Amp.
    - LM78Hxx -- 3 Amps.





## Power Supplies

- Linear Voltage Regulators.
  - Drop-out point.
    - A minimum voltage must be maintained across the pass transistor ( $V_{in} - V_{Out}$ ) to provide regulation.
    - Drop-out point = minimum value of ( $V_{in} - V_{Out}$ ) for regulation to be maintained.



## Power Supplies

- Linear Voltage Regulators.
  - Efficiency.
    - Both shunt & series regulators dissipate a significant amount of power as heat.
      - Series regulators are more efficient because only current required by the load is drawn.
    - Efficiency =  $100\% \times P_{Out} / P_{in}$
    - Power lost as heat in pass transistor =  $(V_{in} - V_{Out}) \times I_L$



## Power Supplies

- Battery Charging Regulators.
  - Special types of regulators called “charge controllers” are used to charge re-chargeable batteries.
    - Required to prevent over-charging or damaging the battery being charged.
    - Type of regulator depends on chemistry of battery being charged.
      - Voltage regulator – Lead-Acid.
      - Current regulator – Ni-Cd, NiMh.



## Power Supplies


- Switching Regulators
  - AC input is rectified & switched on/off at a high frequency.
    - Pulse width is varied to maintain constant average voltage.
  - A transformer changes the voltage level.
  - Output from transformer is rectified & filtered.
  - Output is sampled & compared to a reference.
  - Difference is used to control the pulse width.





## Power Supplies

- Switching Regulators

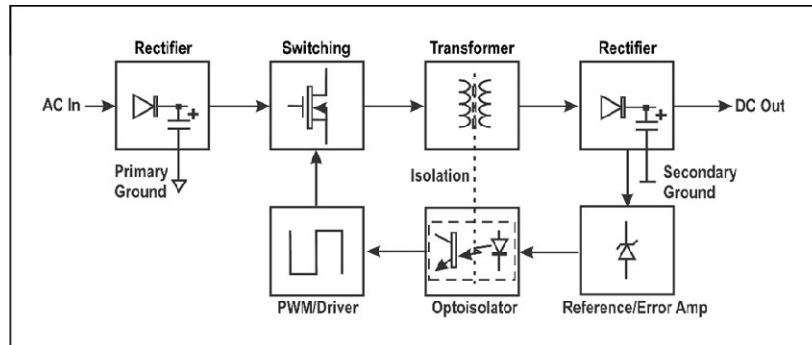

## Power Supplies

- Switching Regulators

- More efficient than linear regulators.
  - Regulation accomplished by varying duty-cycle of input power rather than by dissipating excess power as heat.
- Smaller, lighter, & less expensive than linear regulators.
  - High switching rate allows use of smaller transformers & filter components.

**E7D01 -- What is one characteristic of a linear electronic voltage regulator?**

- A. It has a ramp voltage as its output
- B. It eliminates the need for a pass transistor
- C. The control element duty cycle is proportional to the line or load conditions
- D. The conduction of a control element is varied to maintain a constant output voltage

**E7D02 -- What is one characteristic of a switching electronic voltage regulator?**

- A. The resistance of a control element is varied in direct proportion to the line voltage or load current
- B. It is generally less efficient than a linear regulator
- C. The control device's duty cycle is controlled to produce a constant average output voltage
- D. It gives a ramp voltage at its output

**E7D03 -- What device is typically used as a stable reference voltage in a linear voltage regulator?**

- A. A Zener diode
- B. A tunnel diode
- C. An SCR
- D. A varactor diode

**E7D04 -- Which of the following types of linear voltage regulator usually make the most efficient use of the primary power source?**


- A. A series current source
- B. A series regulator
- C. A shunt regulator
- D. A shunt current source

**E7D05 -- Which of the following types of linear voltage regulator places a constant load on the unregulated voltage source?**

- A. A constant current source
- B. A series regulator
- C. A shunt current source
- D. A shunt regulator


**E7D06 -- What is the purpose of Q1 in the circuit shown in Figure E7-3?**

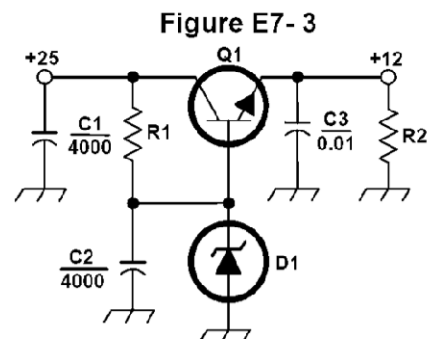- A. It provides negative feedback to improve regulation
- B. It provides a constant load for the voltage source
- C. It increases the current-handling capability of the regulator
- D. It provides D1 with current



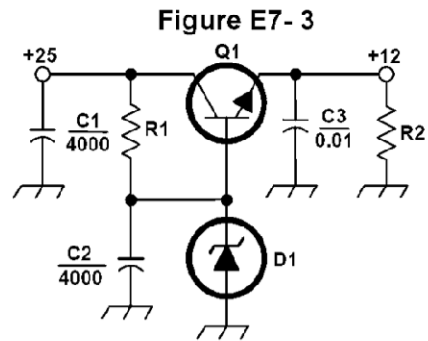
**E7D07 -- What is the purpose of C2 in the circuit shown in Figure E7-3?**

- ➔ A. It bypasses hum around D1
- B. It is a brute force filter for the output
- C. To self-resonate at the hum frequency
- D. To provide fixed DC bias for Q1



**E7D08 -- What type of circuit is shown in Figure E7-3?**

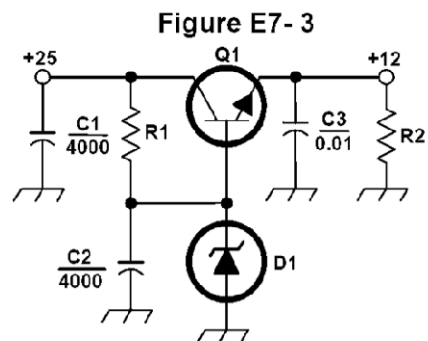- A. Switching voltage regulator
- B. Grounded emitter amplifier
- ➔ C. Linear voltage regulator
- D. Emitter follower



**E7D09 -- What is the main reason to use a charge controller with a solar power system?**

- A. Prevention of battery undercharge
- B. Control of electrolyte levels during battery discharge
- C. Prevention of battery damage due to overcharge
- D. Matching of day and night charge rates

**E7D10 -- What is the primary reason that a high-frequency switching type high voltage power supply can be both less expensive and lighter in weight than a conventional power supply?**

- A. The inverter design does not require any output filtering
- B. It uses a diode bridge rectifier for increased output
- C. The high frequency inverter design uses much smaller transformers and filter components for an equivalent power output
- D. It uses a large power factor compensation capacitor to create free power from the unused portion of the AC cycle

**E7D11 -- What circuit element is controlled by a series analog voltage regulator to maintain a constant output voltage?**

- A. Reference voltage
- B. Switching inductance
- C. Error amplifier
- D. Pass transistor

**E7D12 -- What is the drop-out voltage of an analog voltage regulator?**

- A. Minimum input voltage for rated power dissipation
- B. Maximum amount that the output voltage drops when the input voltage is varied over its specified range
- C. Minimum input-to-output voltage required to maintain regulation
- D. Maximum amount that the output voltage may decrease at rated load


**E7D13 -- What is the equation for calculating power dissipation by a series connected linear voltage regulator?**

- A. Input voltage multiplied by input current
- B. Input voltage divided by output current
- ➔ C. Voltage difference from input to output multiplied by output current
- D. Output voltage multiplied by output current


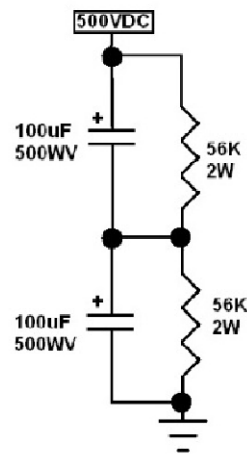
## Power Supplies

- High Voltage Techniques.
  - Bleeder resistor.
    - Discharges capacitors when power is turned off.
    - Improves voltage regulation by providing a minimum load current.
  - Voltage equalizing resistors.
    - Equalizes voltages across filter capacitors in series.







## Power Supplies

- High Voltage Techniques.
  - Step-start.
    - Resistor in series with transformer primary.
    - Relay shorts resistor after specified time.
    - Limits in-rush current.
    - Reduces stress on rectifiers & filter capacitors by limiting in-rush current.
      - Capacitors charge more slowly.

**E7D14 -- What is one purpose of a "bleeder" resistor in a conventional unregulated power supply?**

- A. To cut down on waste heat generated by the power supply
- B. To balance the low-voltage filament windings
- ➔ C. To improve output voltage regulation
- D. To boost the amount of output current

**E7D15 -- What is the purpose of a "step-start" circuit in a high-voltage power supply?**

- A. To provide a dual-voltage output for reduced power applications
- B. To compensate for variations of the incoming line voltage
- C. To allow for remote control of the power supply
- ➔ D. To allow the filter capacitors to charge gradually

**E7D16 -- When several electrolytic filter capacitors are connected in series to increase the operating voltage of a power supply filter circuit, why should resistors be connected across each capacitor?**

- A. To equalize, as much as possible, the voltage drop across each capacitor
- B. To provide a safety bleeder to discharge the capacitors when the supply is off
- C. To provide a minimum load current to reduce voltage excursions at light loads
- ➔ D. All of these choices are correct



# Questions?

